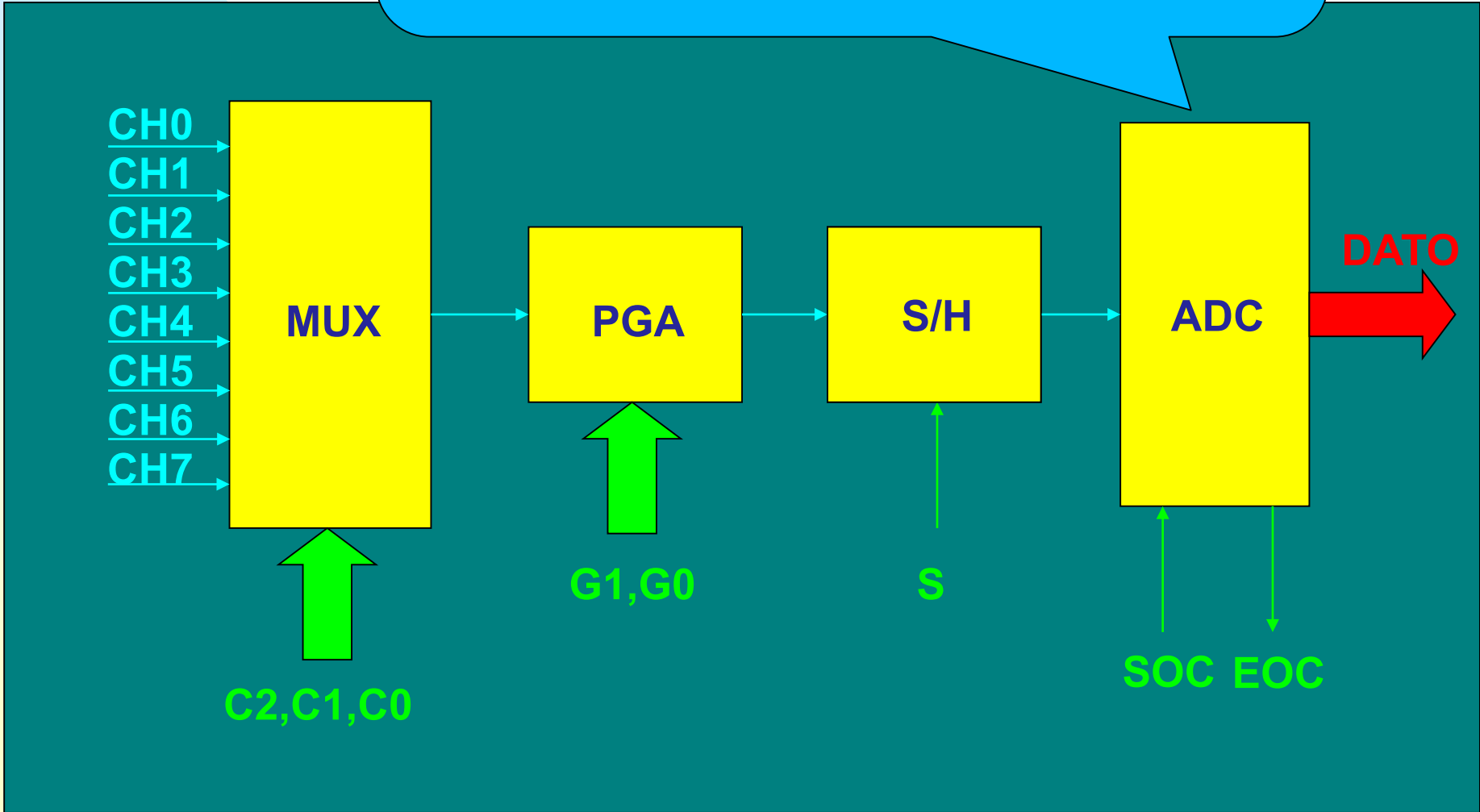


# Analog/Digital Converters

---

Luis Zorzano Martínez

# Analog/Digital Converters



# Analog/Digital Converters


---

Definición

Tipos de ADCs

Aplicaciones

# Analog/Digital Converters

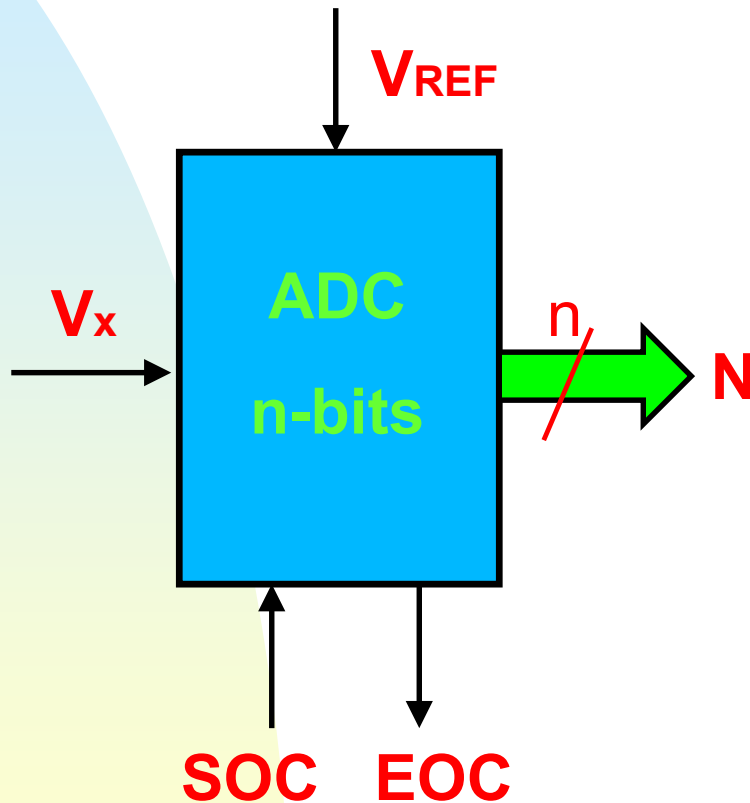


ADC unipolar

$$N = \text{round} \left( \frac{V_x}{V_{REF}} 2^n \right)$$

ADC bipolar

$$N = \text{round} \left( \frac{V_x - (-V_{REF})}{2V_{REF}} 2^n \right)$$

# Analog/Digital Converters

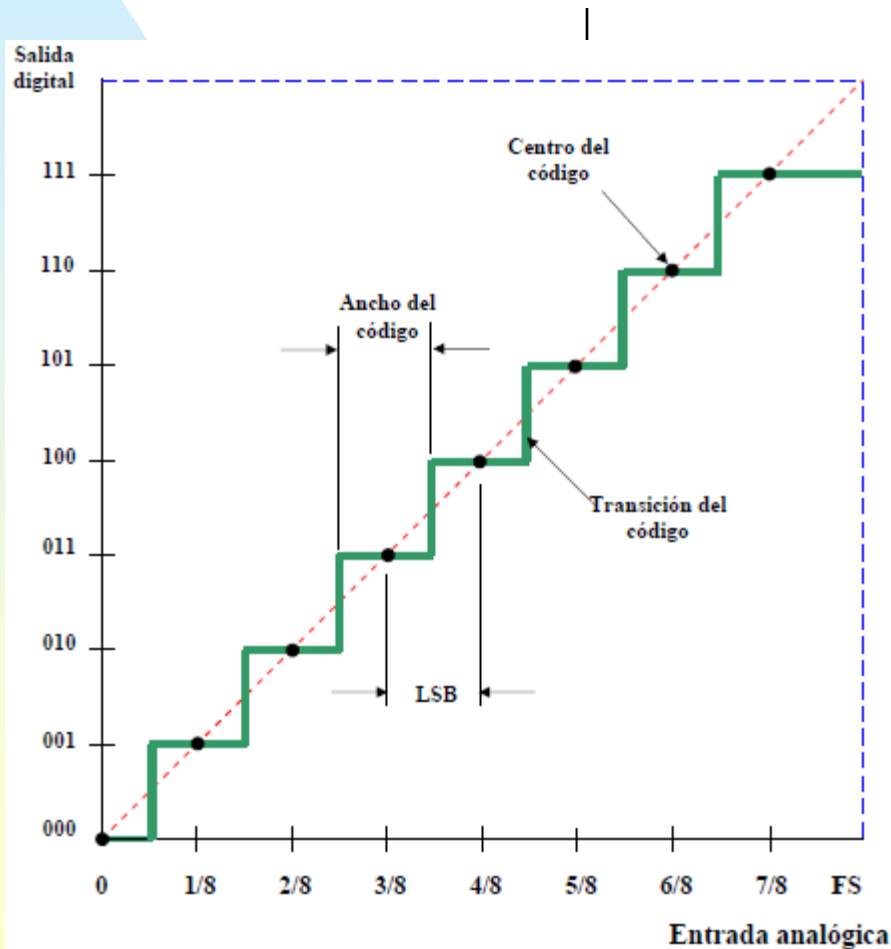

## CÓDIGOS UNIPOLARES

- CÓDIGO BINARIO NATURAL
- CÓDIGO BINARIO INVERTIDO
- CÓDIGO BCD
- CODIGO GRAY

$$N = \text{round} \left( \frac{V_x}{V_{REF}} 2^n \right)$$

## CÓDIGOS BIPOLARES

- CÓDIGO BINARIO DECALADO
- CÓDIGO COMPLEMENTO A 2
- CÓDIGO COMPLEMENTO A 1
- CÓDIGO BINARIO+SIGNO

$$N = \text{round} \left( \frac{V_X - (-V_{REF})}{2V_{REF}} 2^n \right)$$

# ADC: Códigos Unipolares

N	BN	BI	BCD	GRAY
15	1111	0000	1 0101	1000
14	1110	0001	1 0100	1001
13	1101	0010	1 0011	1011
12	1100	0011	1 0010	1010
11	1011	0100	1 0001	1110
10	1010	0101	1 0000	1111
9	1001	0110	0 1001	1101
8	1000	0111	0 1000	1100
7	0111	1000	0 0111	0100
6	0110	1001	0 0110	0101
5	0101	1010	0 0101	0111
4	0100	1011	0 0100	0110
3	0011	1100	0 0011	0010
2	0010	1101	0 0010	0011
1	0001	1110	0 0001	0001
0	0000	1111	0 0000	0000

## CÓDIGOS UNIPOLARES

- CÓDIGO BINARIO NATURAL
- CÓDIGO BINARIO INVERTIDO
- CÓDIGO BCD
- CODIGO GRAY

$$N = \text{round} \left( \frac{V_x}{V_{REF}} 2^n \right)$$

# ADC: Códigos Bipolares

N	B+S	BO	CA2	CA1
7	1111	1111	0111	0111
6	1110	1110	0110	0110
5	1101	1101	0101	0101
4	1100	1100	0100	0100
3	1011	1011	0011	0011
2	1010	1010	0010	0010
1	1001	1001	0001	0001
0	1000	1000	0000	0000
-0	0000			1111
-1	0001	0111	1111	1110
-2	0010	0110	1110	1101
-3	0011	0101	1101	1100
-4	0100	0100	1100	1011
-5	0101	0011	1011	1010
-6	0110	0010	1010	1001
-7	0111	0001	1001	1000
-8		0000	1000	


## CÓDIGOS BIPOLARES

- CÓDIGO BINARIO DECALADO (B.O.)
- CÓDIGO COMPLEMENTO A 2
- CÓDIGO COMPLEMENTO A 1
- CÓDIGO BINARIO+SIGNO

$$N = \text{round} \left( \frac{V_X - (-V_{REF})}{2V_{REF}} 2^n \right)$$
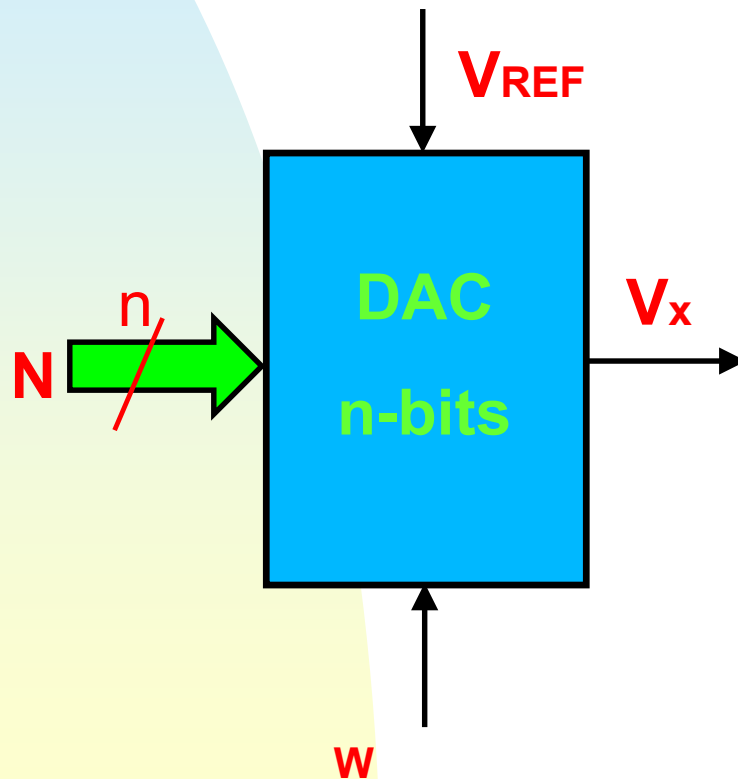
# DAC: antes de los ADCs

- Muchos ADCs incorporan DACs
- DAC: Digital Analog Converter




DAC

$$V_x = \left( \frac{N}{2^n} V_{REF} \right)$$



# DAC con resistencias ponderadas
 
## Convertidor Analógico Digital de 4 bits con resistencias ponderadas





Un convertidor D/A de 4 bits (DAC)  
con entradas ponderadas en binario.

$$V_{sal} = -R_F I_F = -R_F \sum_{i=0}^3 b_i I_i = -R_F \sum_{i=0}^3 b_i \frac{V}{R_i} = -R_F \sum_{i=0}^3 b_i \frac{V}{2^{3-i} R} =$$

$$V_{sal} = -V \frac{R_F}{2^3 R} \sum_{i=0}^3 b_i 2^i = -V \frac{R_F}{2^3 R} N$$

# DAC en escalera R/2R

## DAC en escalera R/2R

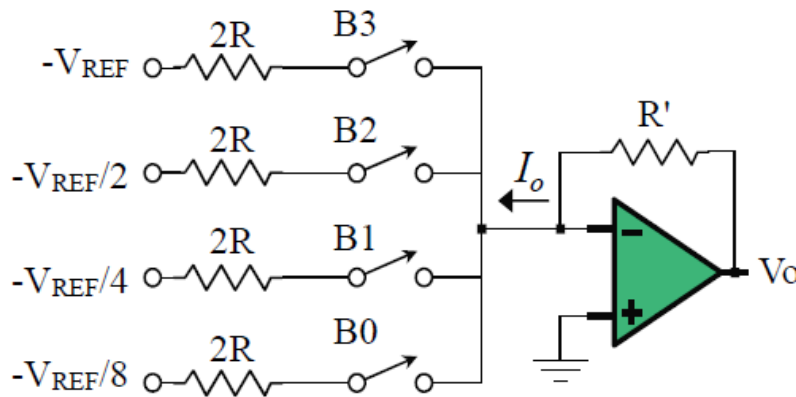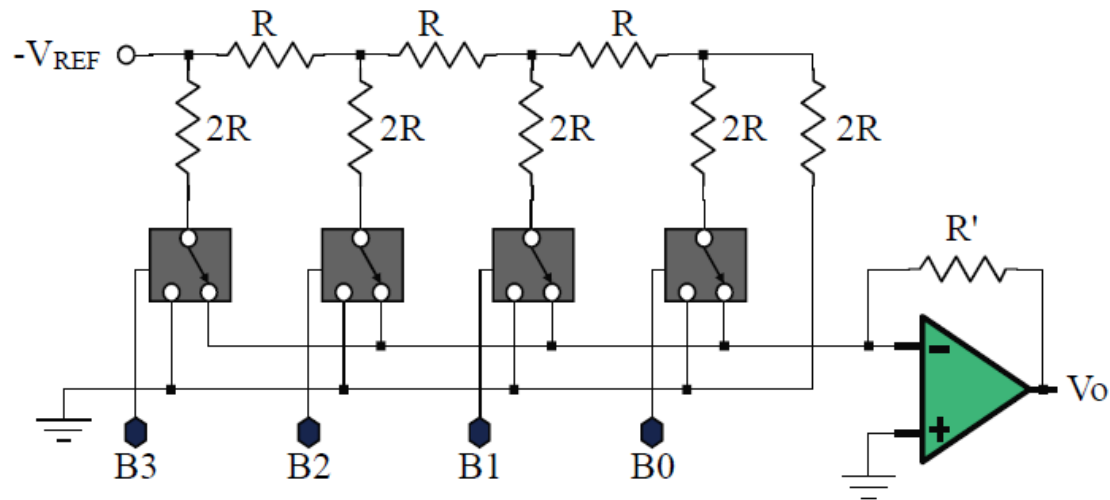


$$I_o = \frac{V_{ref}}{2^n R} \cdot \sum_{i=0}^{n-1} 2^i \cdot B_i$$

$$V_o = \frac{V_{ref}}{2^n} \cdot \sum_{i=0}^{n-1} 2^i \cdot B_i$$


# ADC: Principio básico

Temperatura ambiente

 


ADC de 1 bit

# ADC: Principio básico

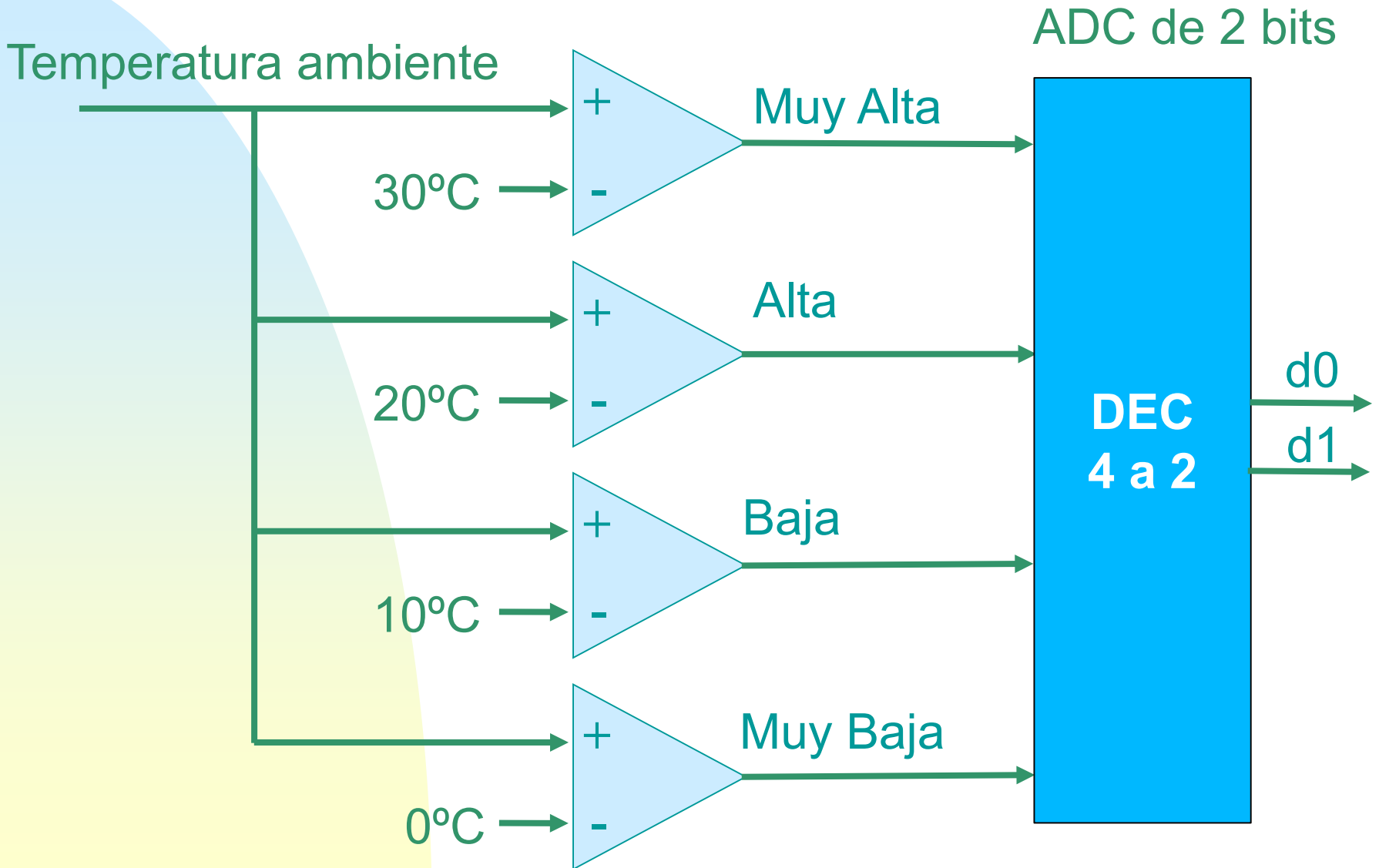


# ADC: Principio básico

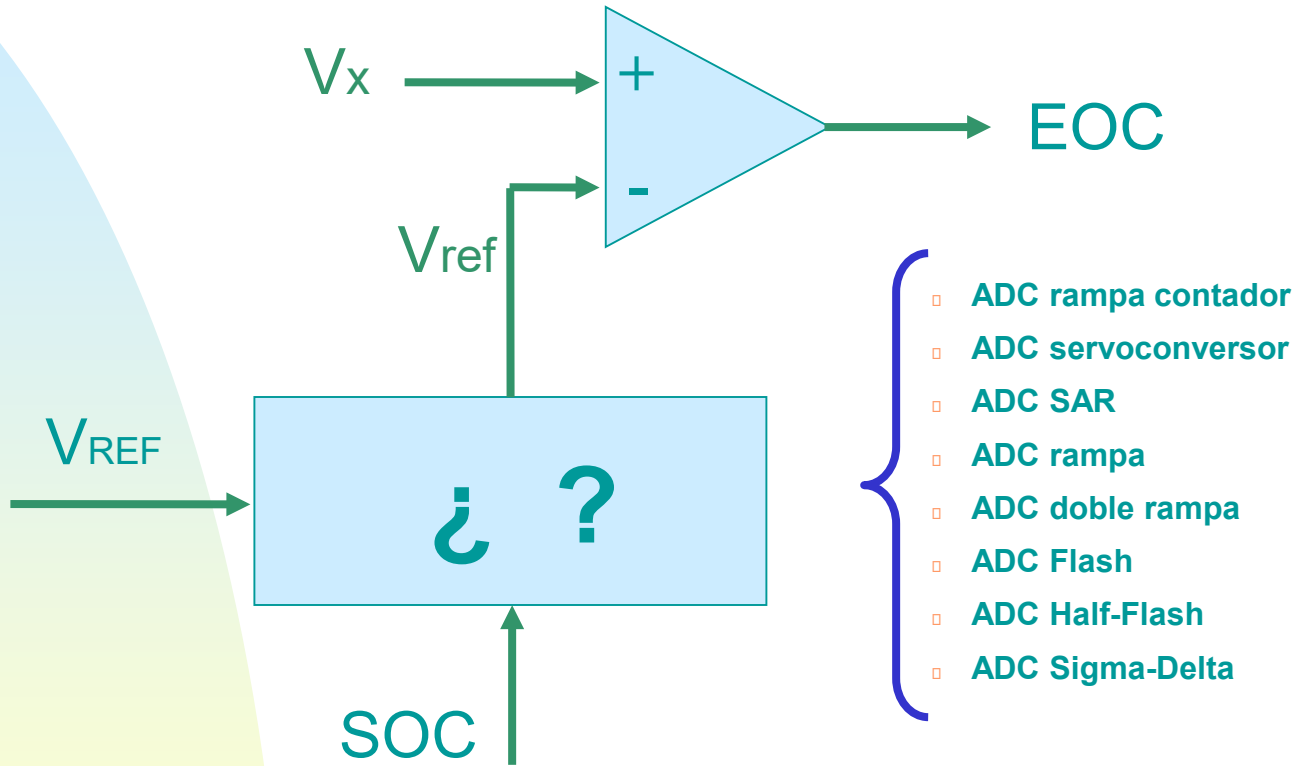

# Tipos de convertidores


- ADC rampa contador
- ADC servoconversor
- ADC SAR
- ADC rampa
- ADC doble rampa
- ADC Flash
- ADC Half-Flash
- ADC Sigma-Delta

# ADC rampa-contador

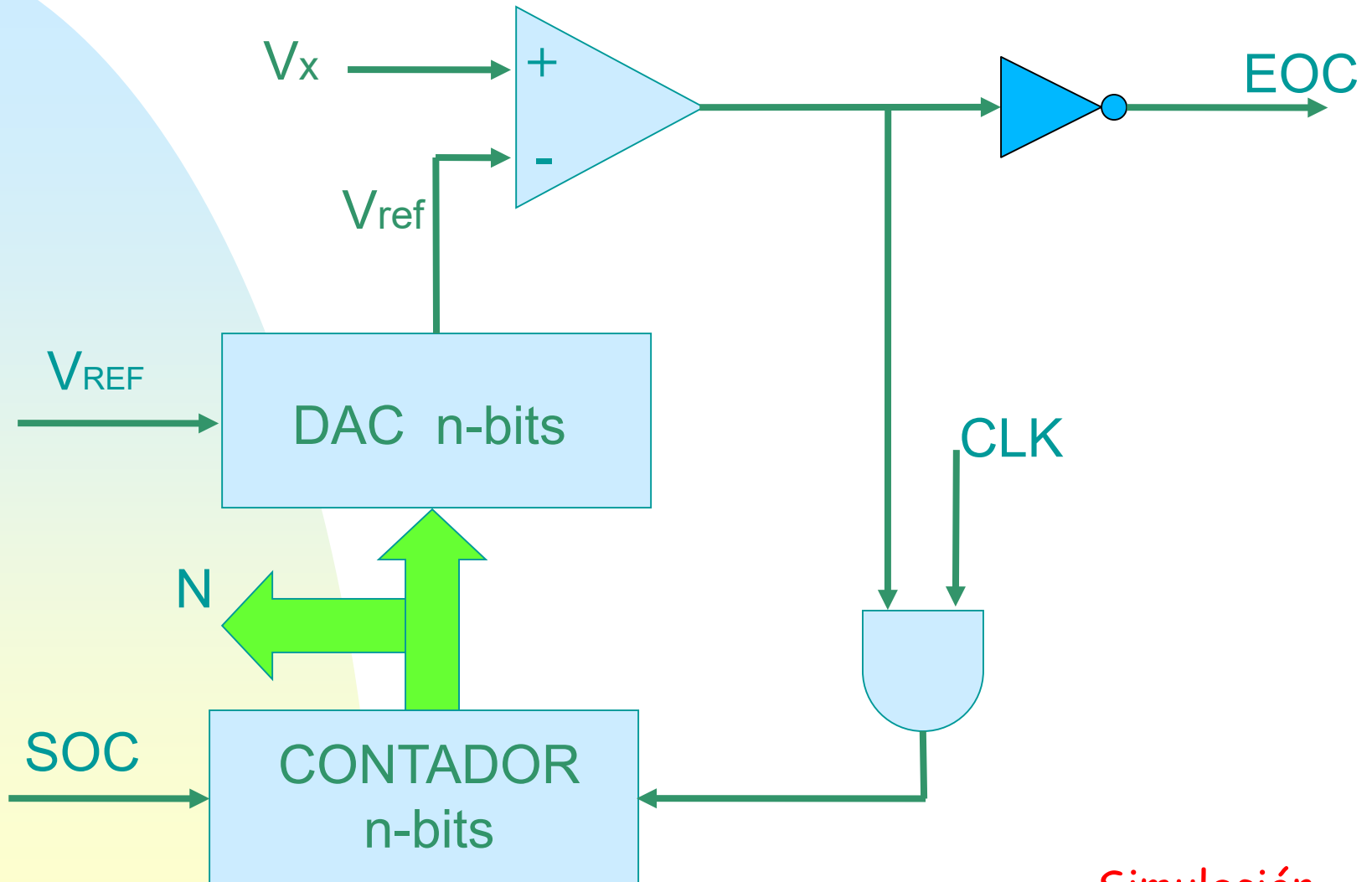


Simulación

# ADC rampa-contador

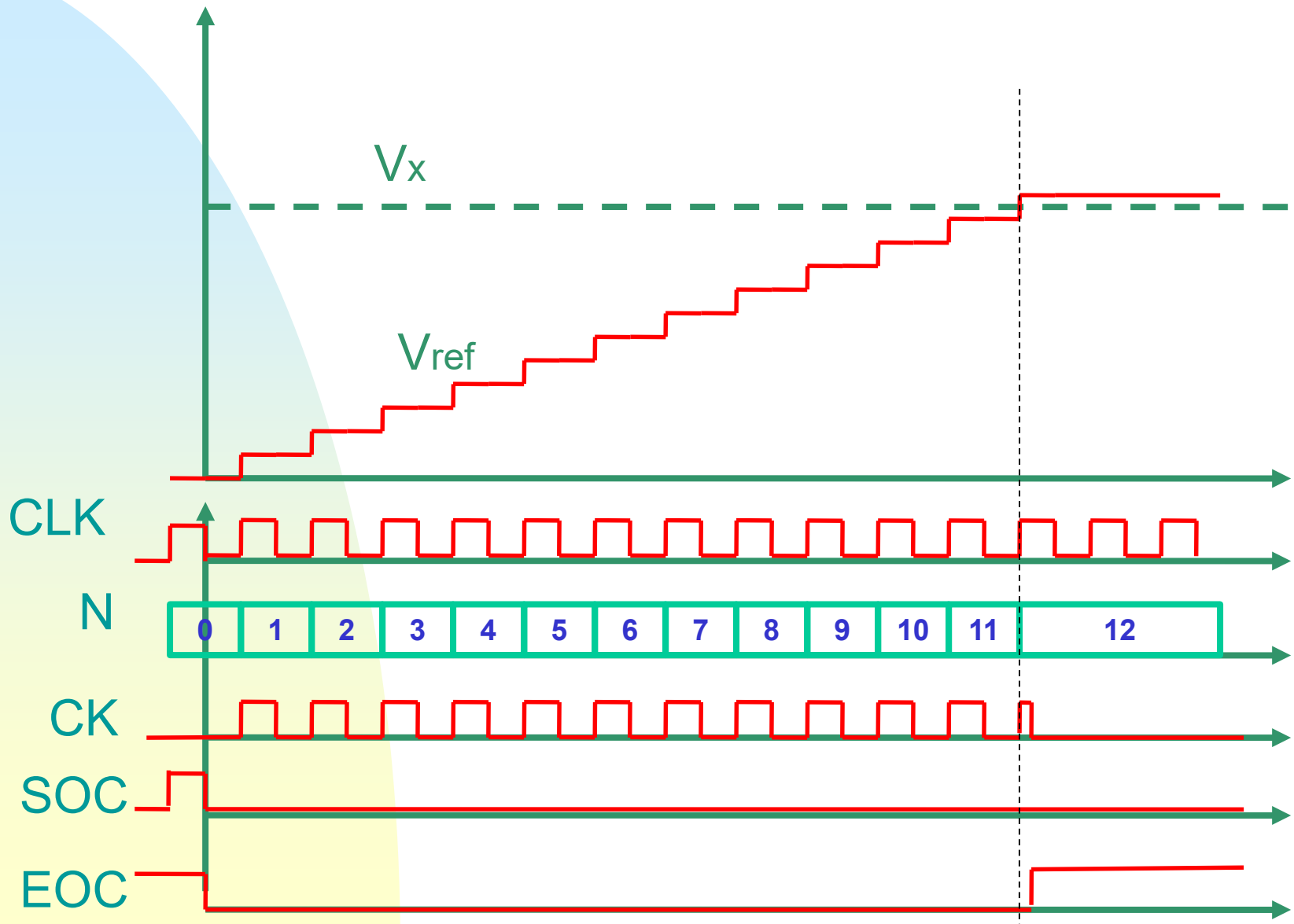




# ADC servoconversor

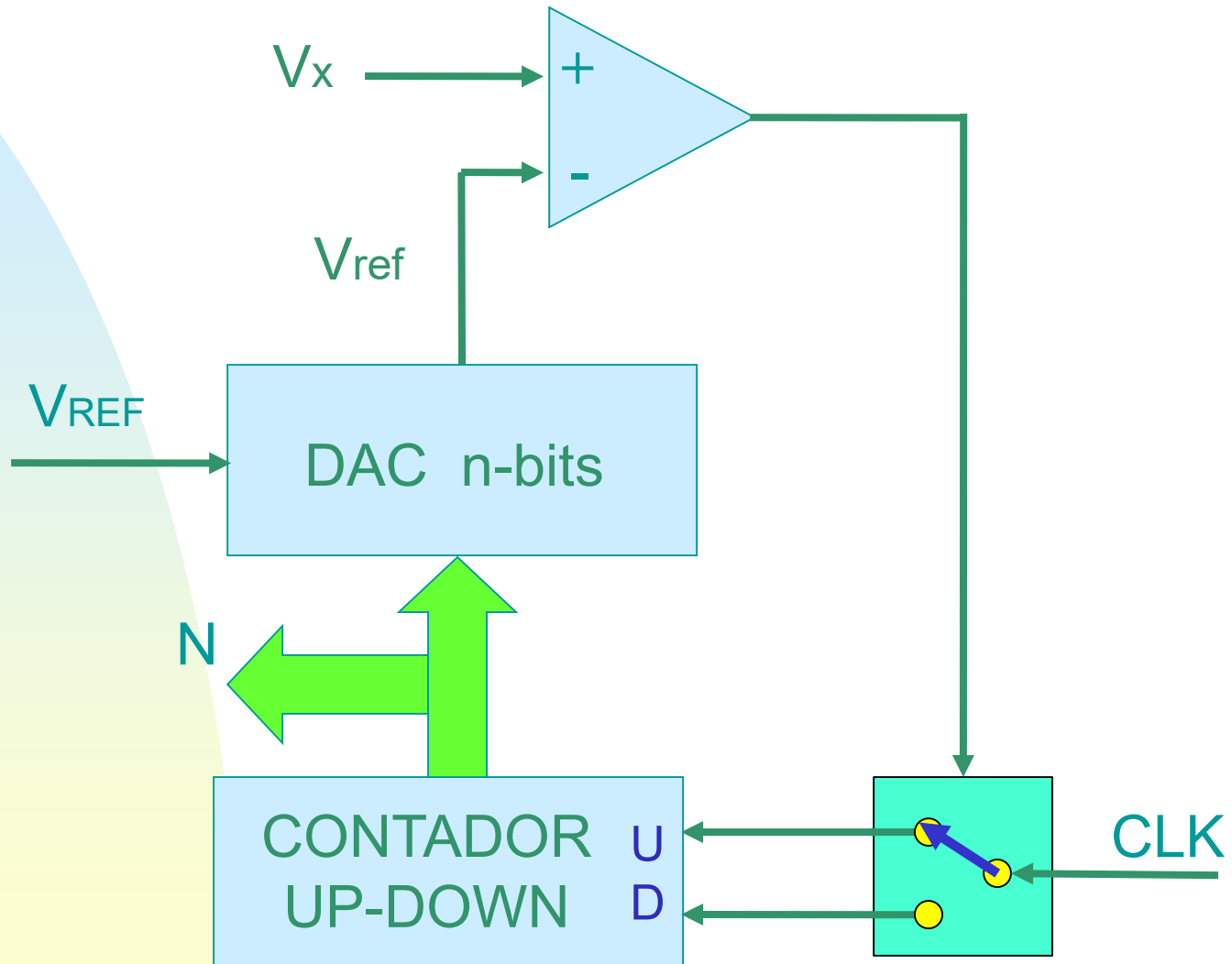


Simulación


# ADC servoconversor

 


# ADC SAR

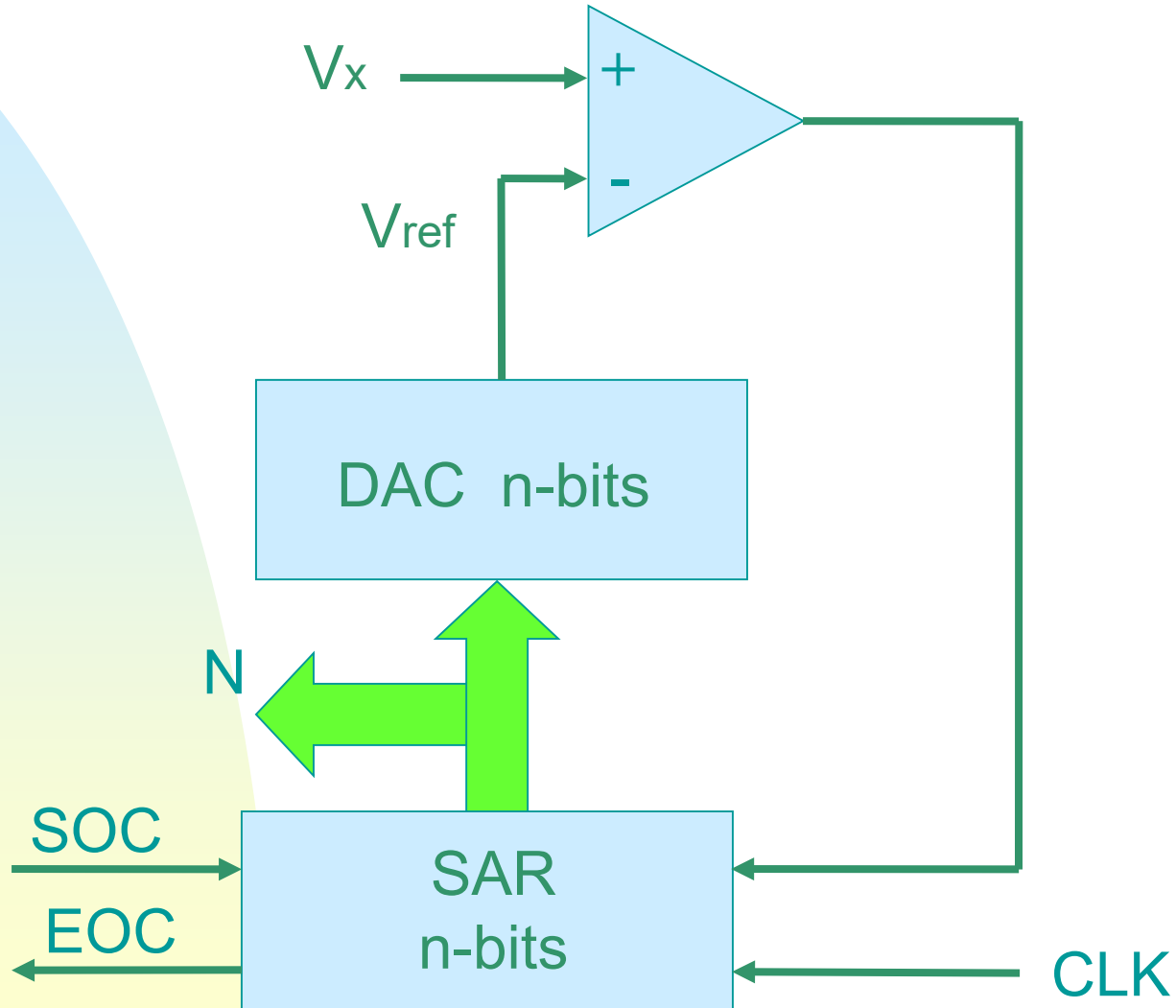

# ADC SAR

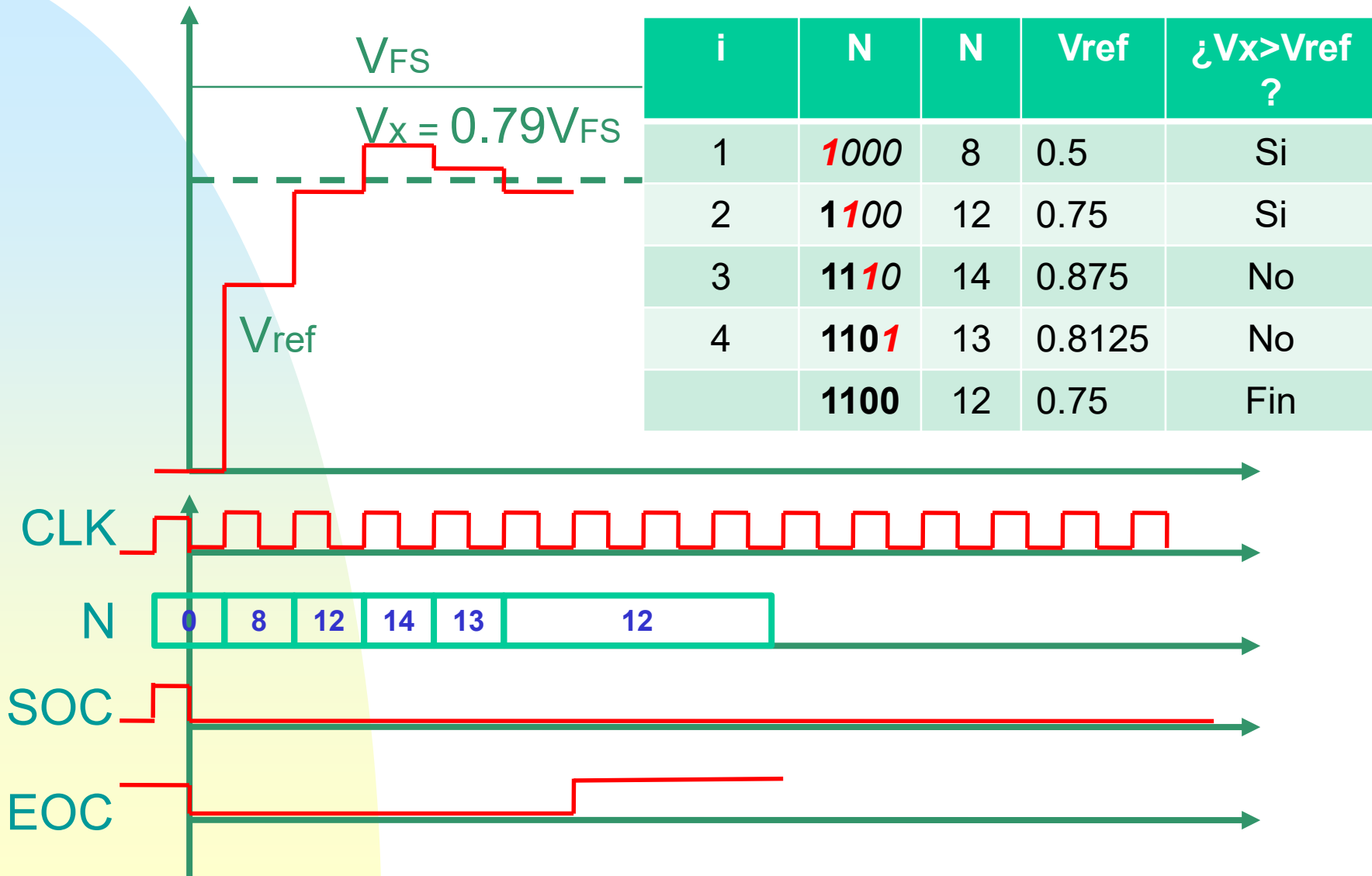

# ADC SAR 8 bits

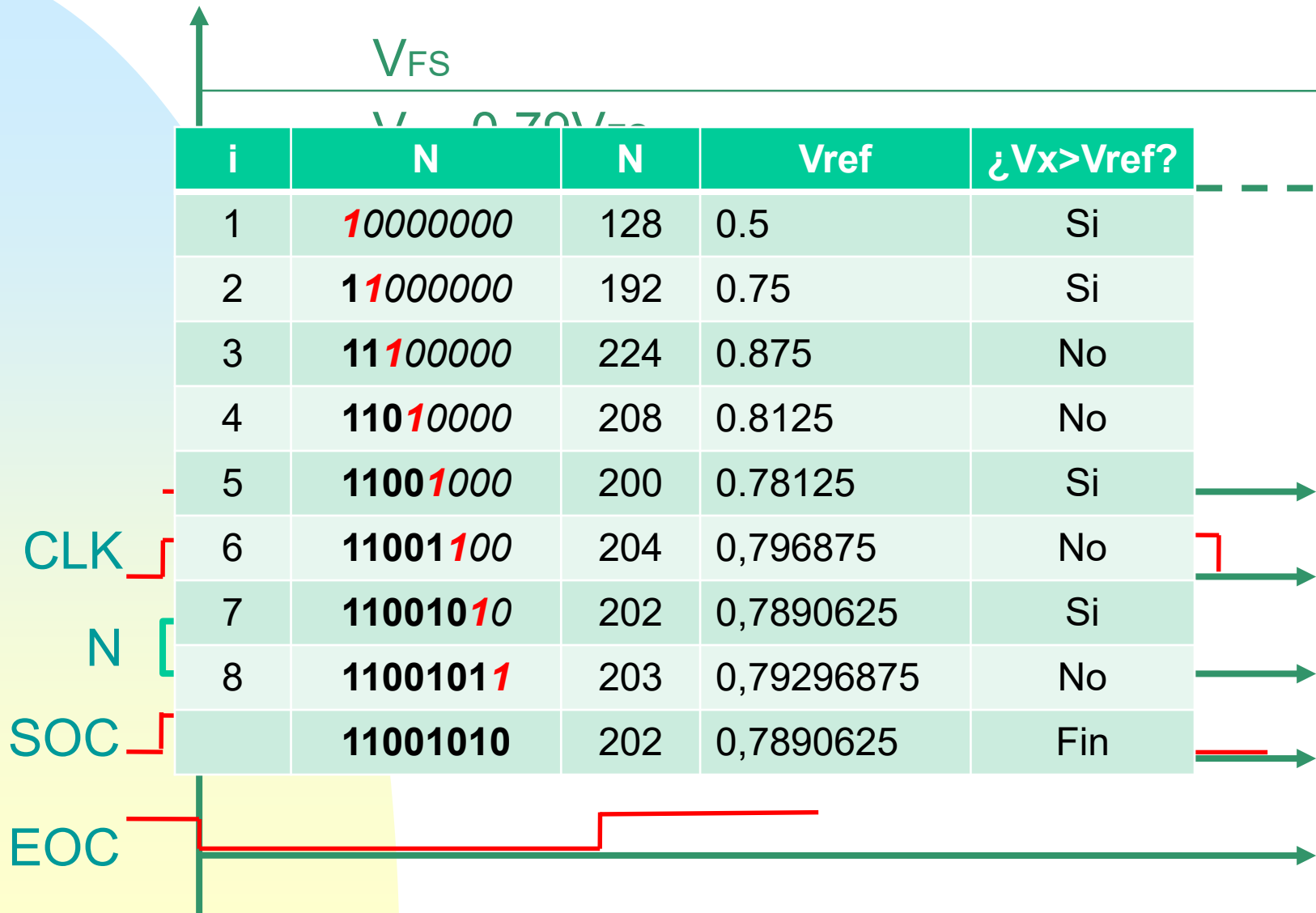

# ADC SAR sc


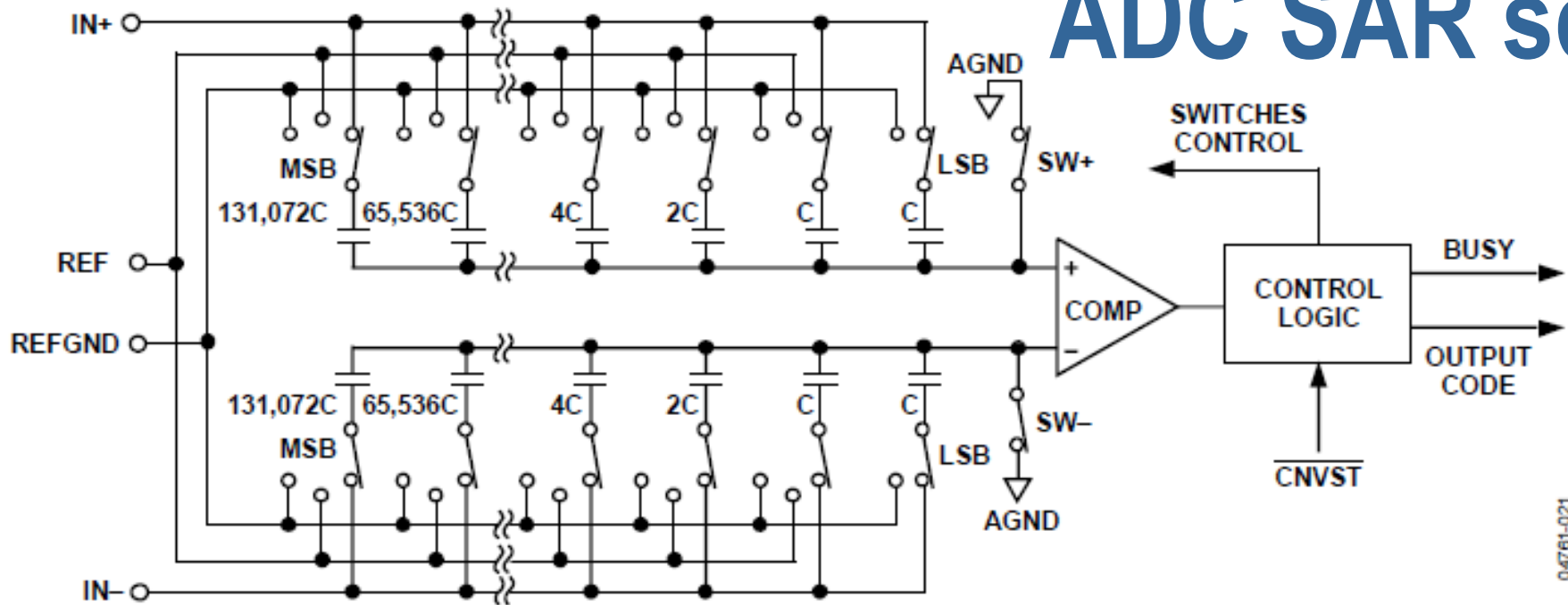


Figure 21. ADC Simplified Schematic

During the acquisition phase, terminals of the array tied to the comparator's input are connected to AGND via SW+ and SW-. All independent switches are connected to the analog inputs. Therefore, the capacitor arrays are used as sampling capacitors and acquire the analog signal on the IN+ and IN- inputs. A conversion phase is initiated once the acquisition phase is complete and the CNVST input goes low. When the conversion phase begins, SW+ and SW- are opened first. The two capacitor arrays are then disconnected from the inputs and connected to the REFGND input. Therefore, the differential voltage between the inputs (IN+ and IN-) captured at the end of the acquisition phase is applied to the comparator inputs, causing the


comparator to become unbalanced. By switching each element of the capacitor array between REFGND and REF, the comparator input varies by binary weighted voltage steps ( $V_{REF}/2$ ,  $V_{REF}/4$  through  $V_{REF}/131072$ ). The control logic toggles these switches, starting with the MSB first, to bring the comparator back into a balanced condition. After the completion of this process, the control logic generates the ADC output code and brings BUSY output low.

# ADC simple rampa

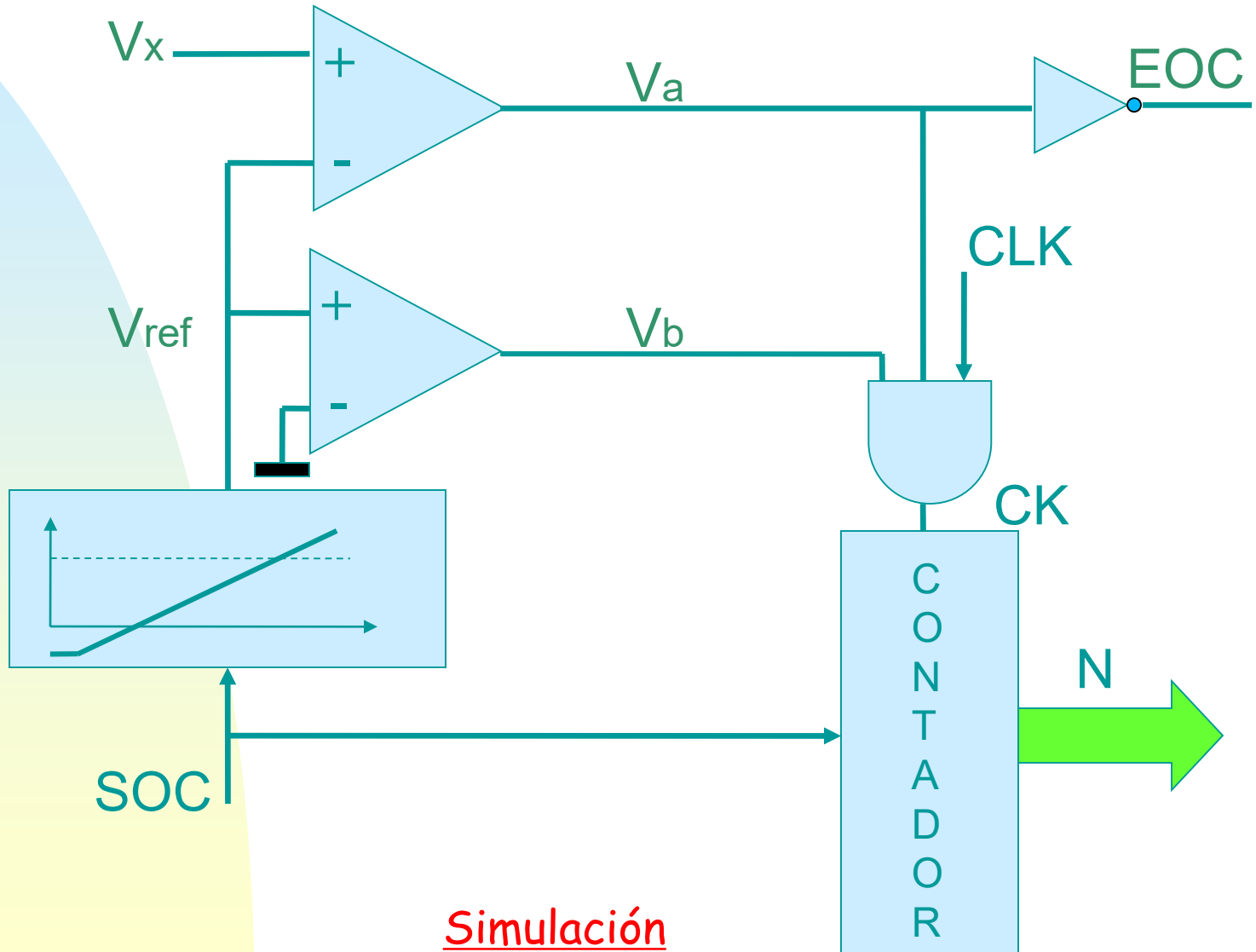


Simulación

# ADC simple rampa

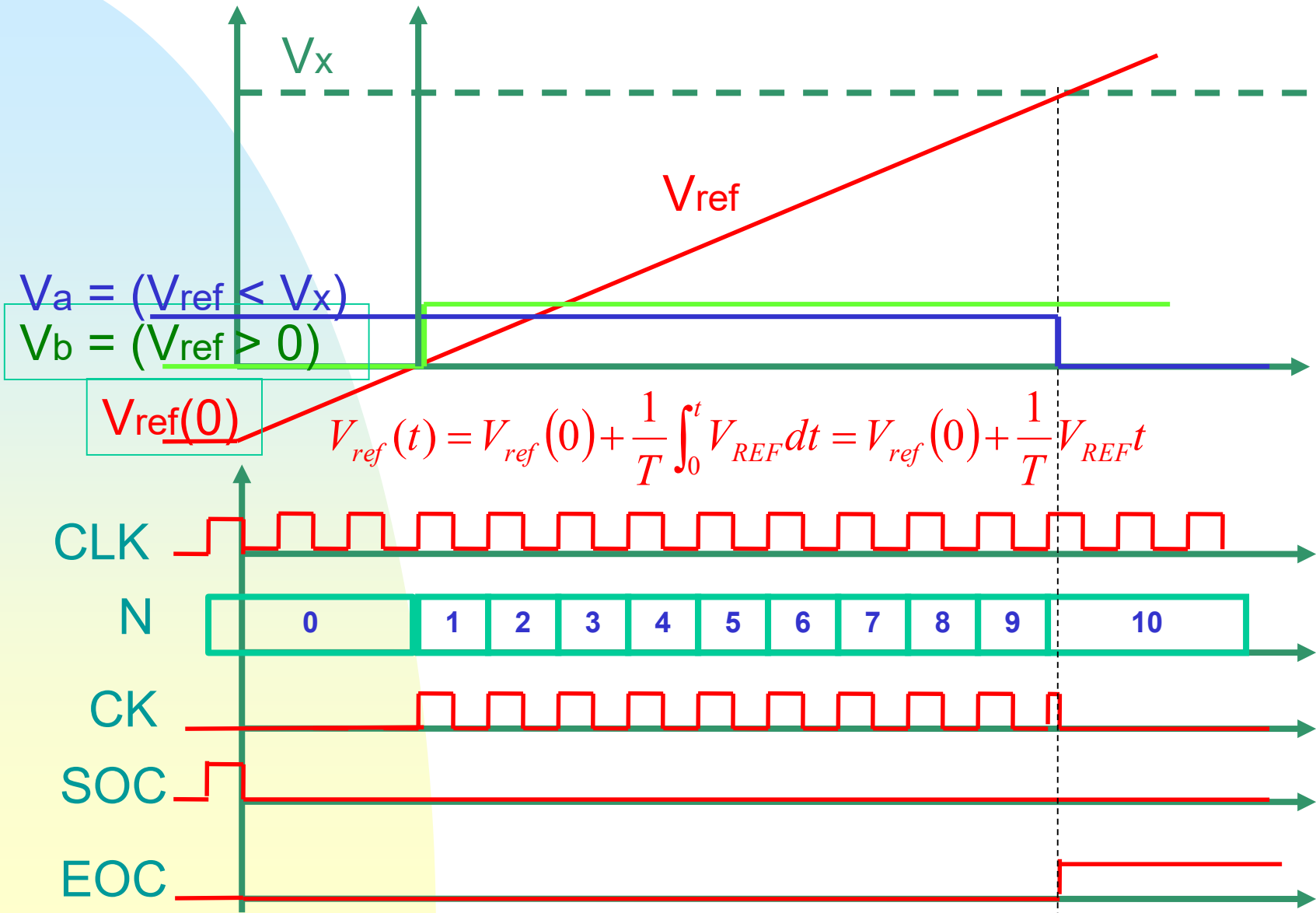




# ADC simple rampa

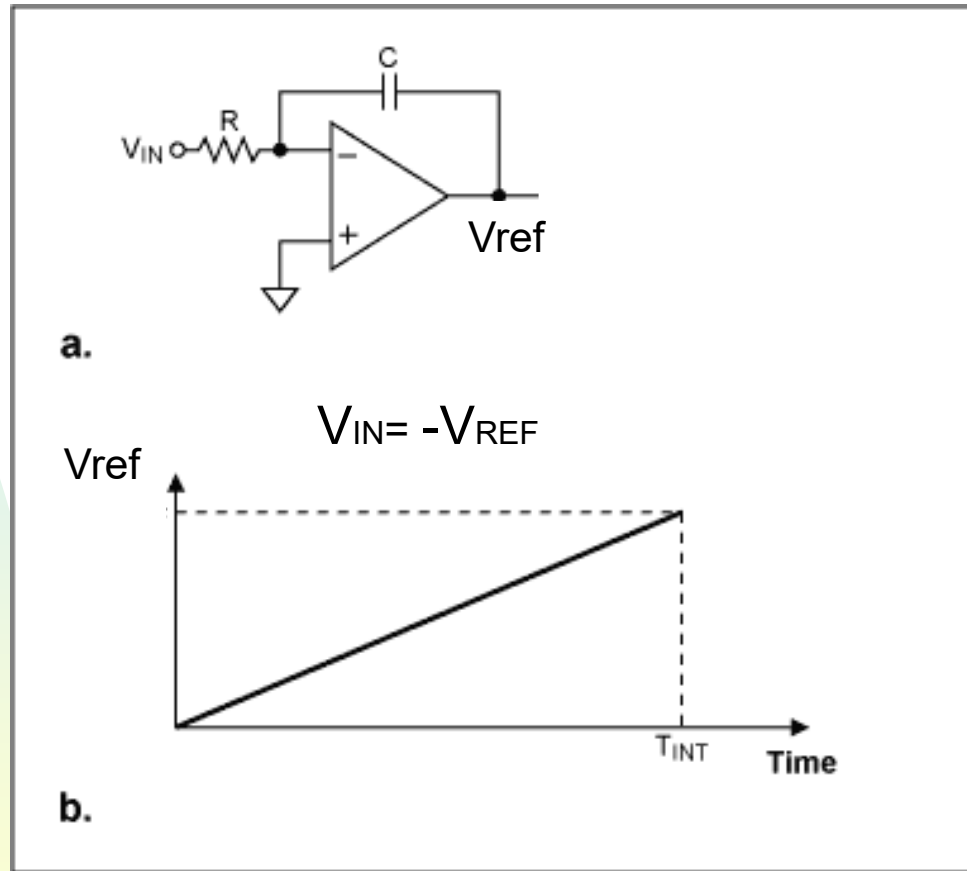

$$V_{ref}(t) = V_{ref}(0) - \frac{1}{RC} \int_0^t V_{IN} dt = V_{ref}(0) + \frac{1}{RC} \int_0^t V_{REF} dt = V_{ref}(0) + \frac{1}{RC} V_{REF} t$$

# ADC simple rampa

 


Ecuación definida en el tiempo de ejecución

$$\left. \begin{aligned}
 V_x &= V_{ref}(t = N \cdot T_{CK}) = \frac{1}{RC} V_{REF} \cdot N \cdot T_{CK} \\
 V_{FS} &= V_{ref}(t = 2^n \cdot T_{CK}) = \frac{1}{RC} V_{REF} \cdot 2^n \cdot T_{CK}
 \end{aligned} \right\} \frac{V_x}{V_{FS}} = \frac{\frac{1}{RC} V_{REF} \cdot N \cdot T_{CK}}{\frac{1}{RC} V_{REF} \cdot 2^n \cdot T_{CK}}$$

Ecuación definida en el tiempo de diseño

$$\frac{V_x}{V_{FS}} = \frac{N}{2^n}; \quad N = 2^n \frac{V_x}{V_{FS}}$$

# ADC doble rampa

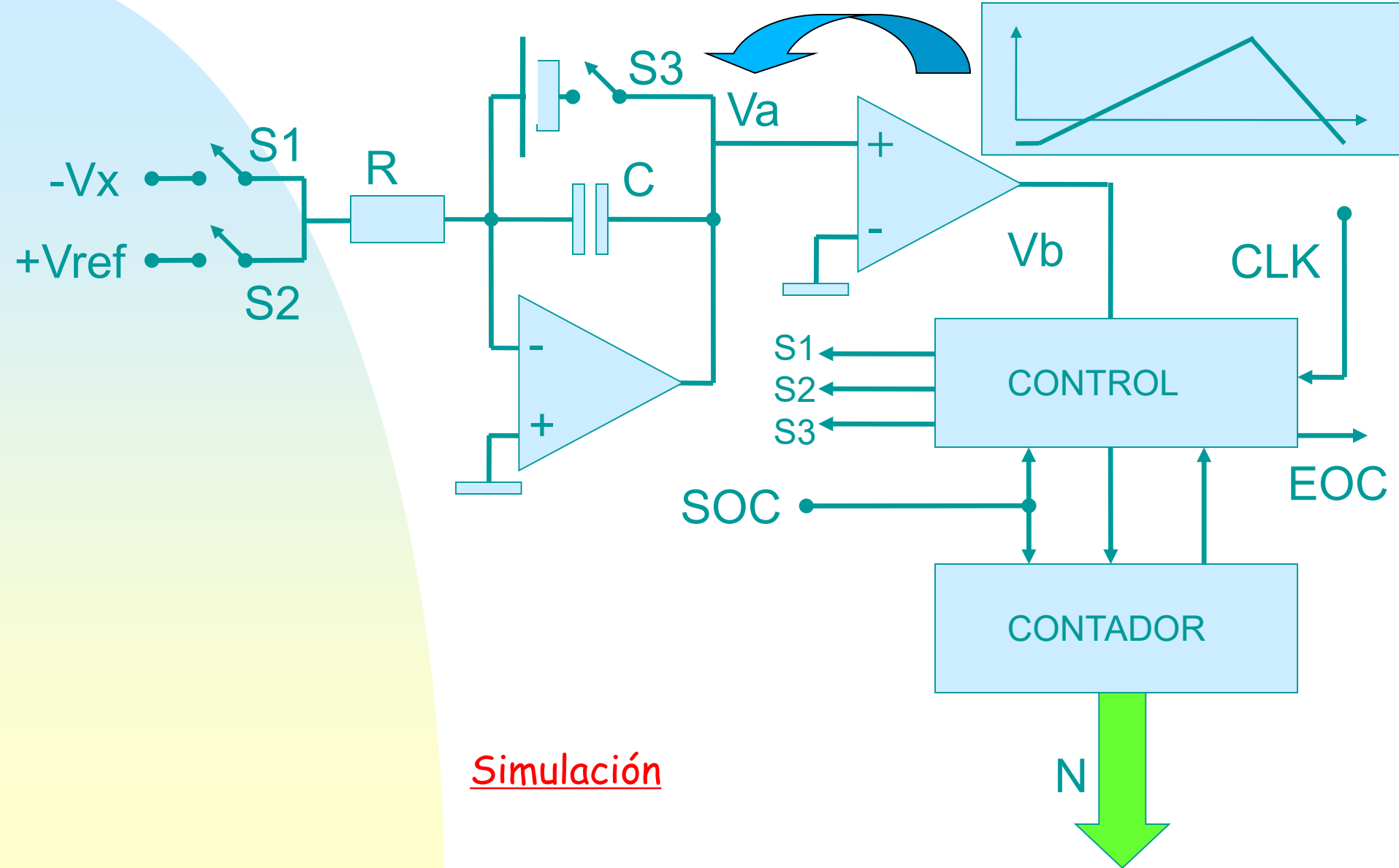



# ADC doble rampa

$$\left. \begin{aligned} V_a &= V_a(0) + \frac{1}{T} \int_0^t V_x dt = 0 + \frac{1}{RC} V_x t \\ V_a &= V_P - \frac{1}{T} \int_0^t V_{REF} dt = V_P - \frac{1}{RC} V_{REF} t \end{aligned} \right\}$$
$$\left. \begin{aligned} V_P &= \frac{1}{RC} V_x 2^n T_{CK} \\ 0 &= V_P - \frac{1}{RC} V_{REF} N \cdot T_{CK} \end{aligned} \right\} \frac{1}{RC} V_x 2^n T_{CK} = \frac{1}{RC} V_{REF} N \cdot T_{CK}$$

$$V_x 2^n = V_{REF} N$$

$$N = \frac{V_x}{V_{REF}} 2^n$$

Diferencia de tiempos  
del orden de ms

# ADC doble rampa (NMRR)

Si  $v_x \neq \text{cte.}$  entonces  $V_a = 0 + \frac{1}{T} \int_0^t v_x dt$

$$V_a = V_P - \frac{1}{T} \int_0^t V_{REF} dt = V_P - \frac{1}{T} V_{REF} t$$

$$V_P = \frac{1}{T} \int_0^{2^n T_{CK}} v_x dt$$

$$0 = V_P - \frac{1}{T} V_{REF} N \cdot T_{CK}$$


$$V_P = \frac{1}{T} \int_0^{2^n T_{CK}} v_x dt = \frac{1}{T} V_{REF} N \cdot T_{CK}$$

$$N = \frac{1}{V_{REF} \cdot T_{CK}} \int_0^{2^n T_{CK}} v_x dt$$

$$N = \frac{2^n}{V_{REF} \cdot 2^n T_{CK}} \int_0^{2^n T_{CK}} v_x dt = \frac{2^n}{V_{REF}} \frac{1}{2^n T_{CK}} \int_0^{2^n T_{CK}} v_x dt = \frac{2^n}{V_{REF}} \overline{V_x}$$
 
# ADC doble rampa (NMRR)

$$N = \frac{2^n}{V_{REF}} \frac{1}{T_i} \int_0^{T_i} v_x dt = \frac{2^n}{V_{REF}} \frac{1}{T_i} \int_0^{T_i} [V_{DC} + V_N \cdot \sin(2\pi ft)] dt$$



# Ejemplo de ADC doble rampa

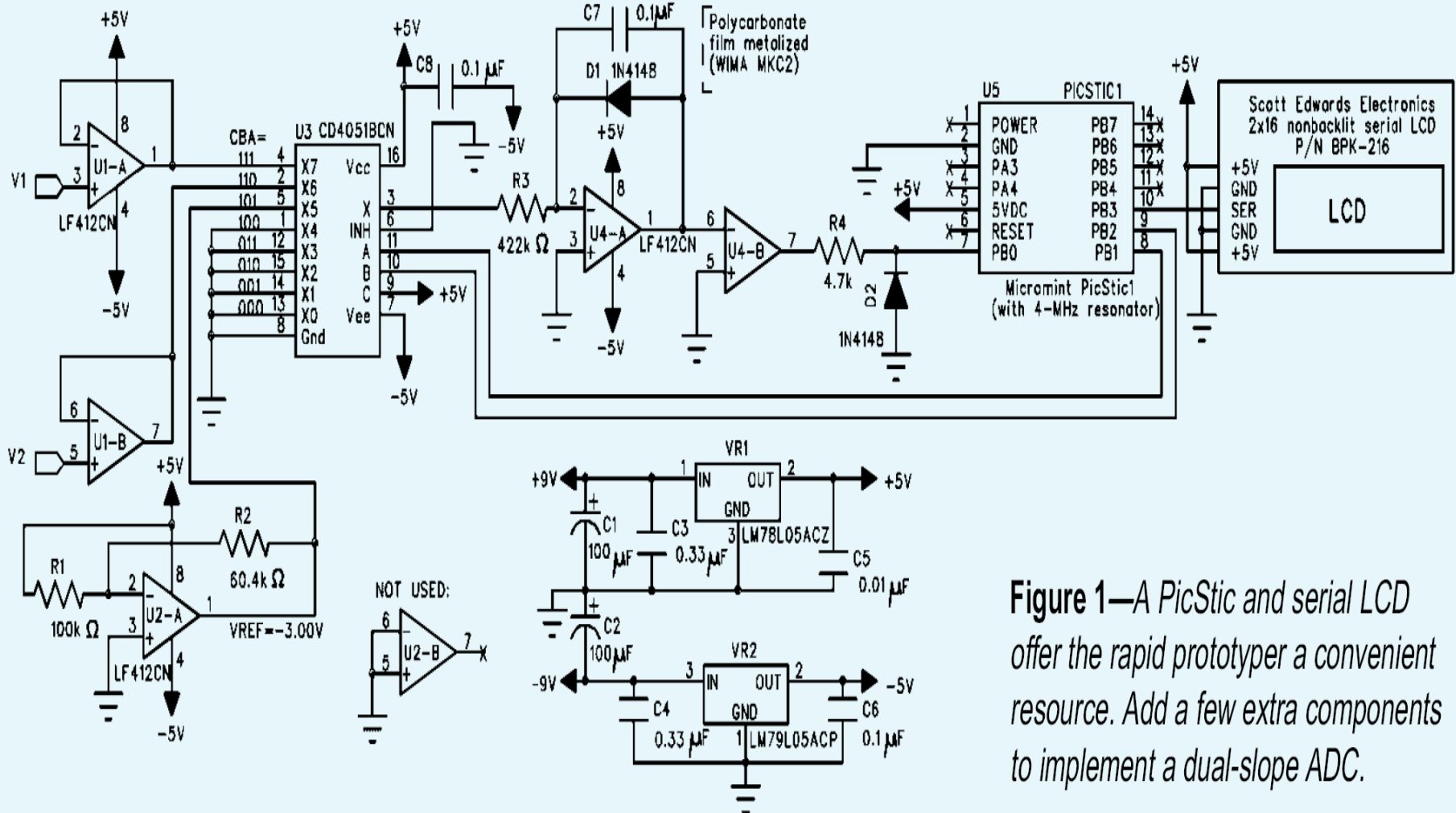


Figure 1—A PicStic and serial LCD offer the rapid prototyper a convenient resource. Add a few extra components to implement a dual-slope ADC.



# ADC doble rampa

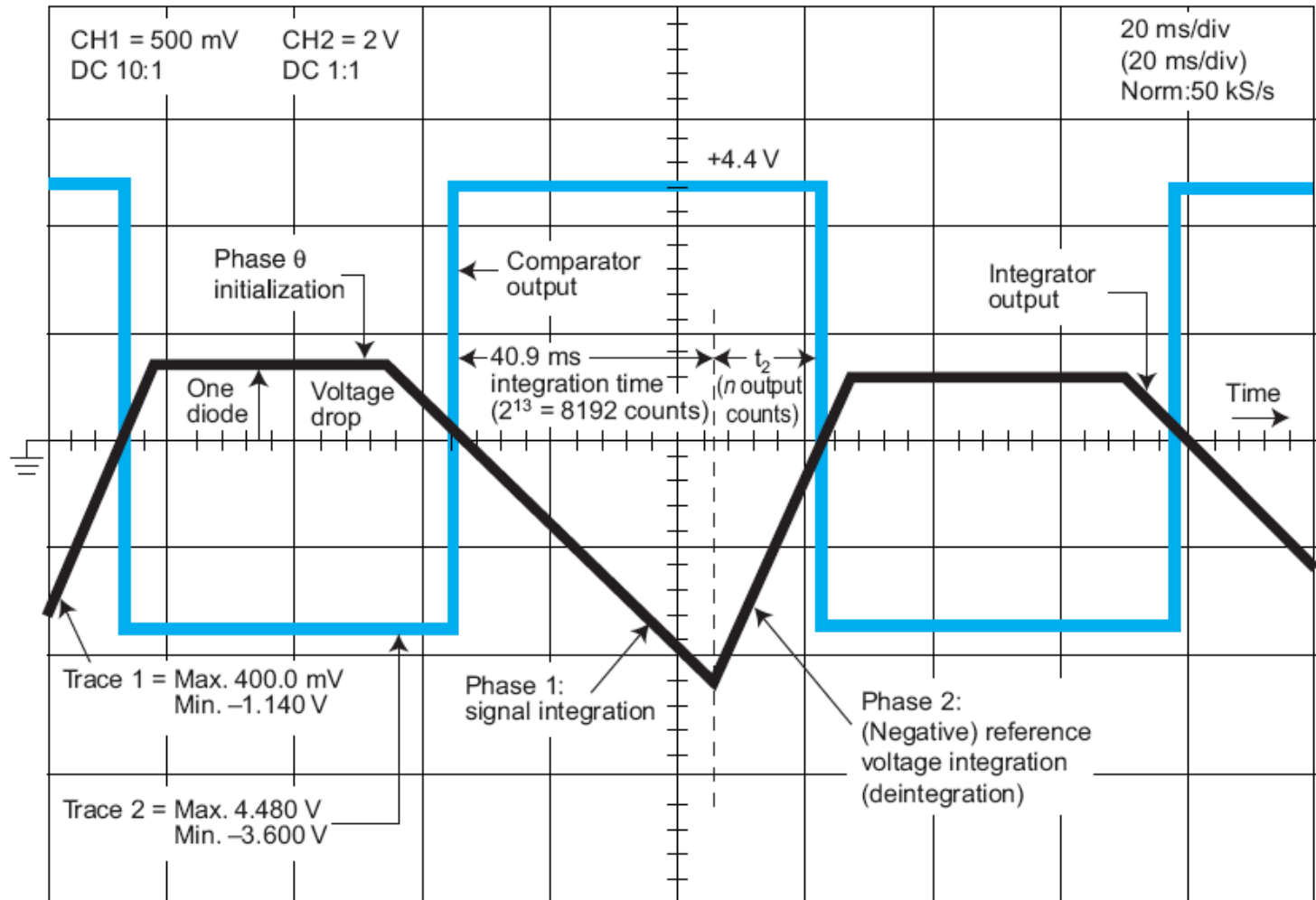


Figure 2—Integration count begins when the falling voltage ramp passes through zero and ends after 8192 counts. The deintegration count then begins, ending only when the rising voltage ramp again passes through zero.

# ADC doble rampa


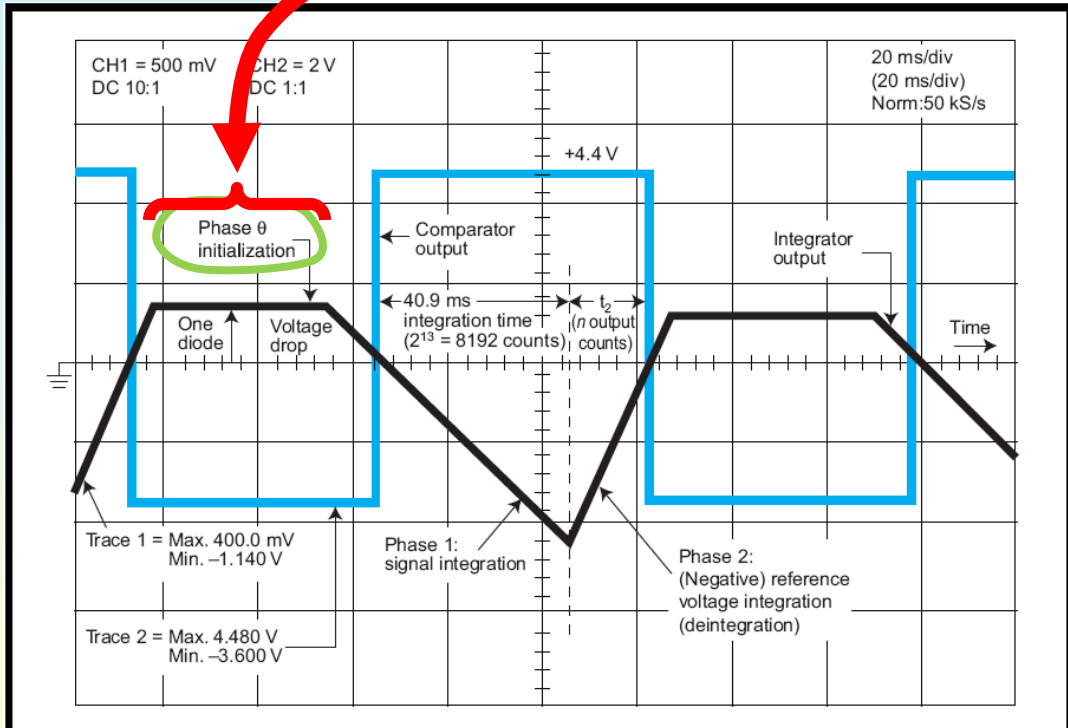


Figure 2—Integration count begins when the falling voltage ramp passes through zero and ends after 8192 counts. The deintegration count then begins, ending only when the rising voltage ramp again passes through zero.

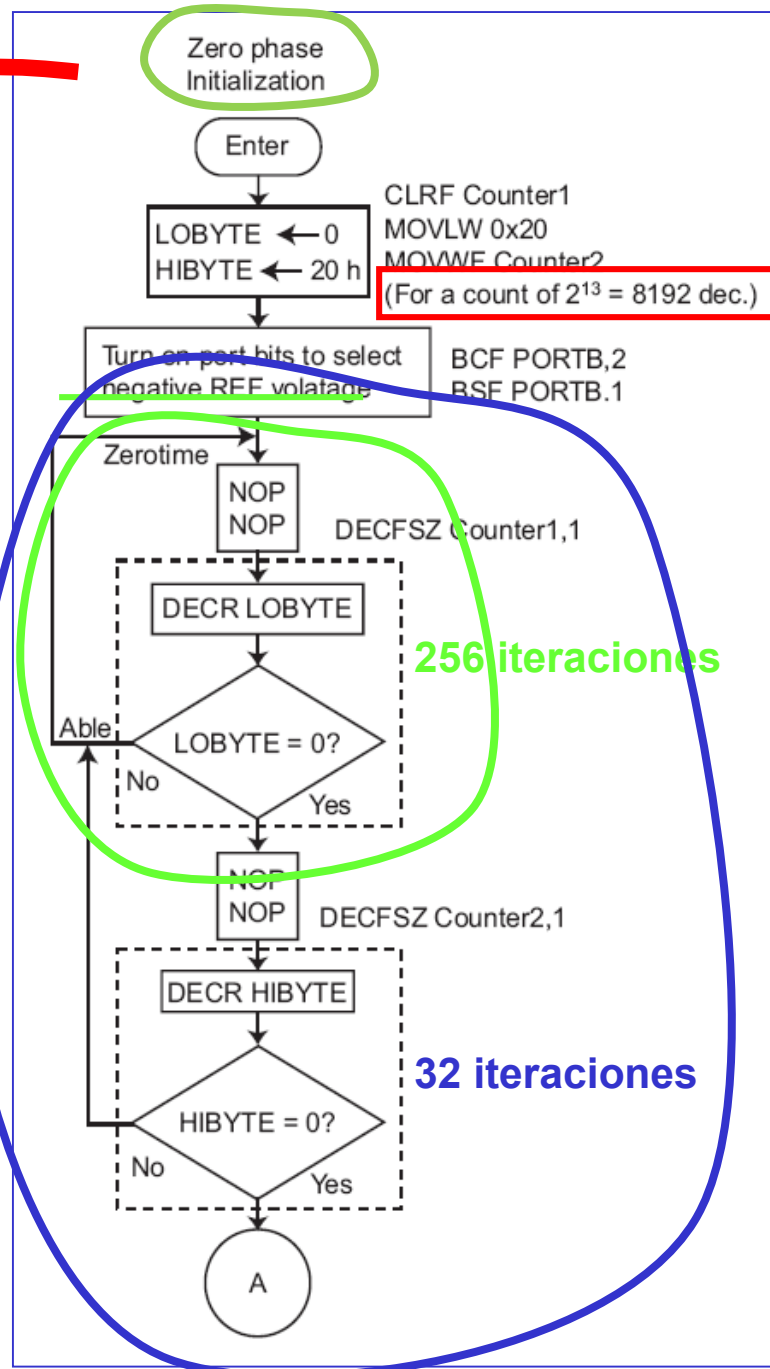

# ADC doble rampa


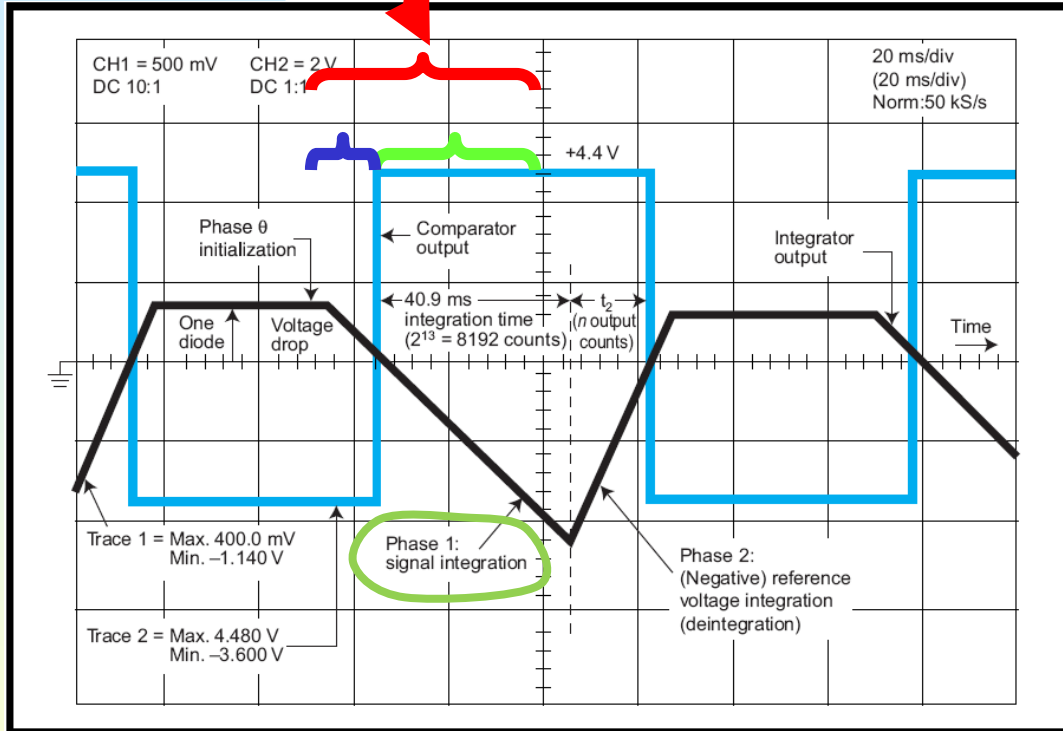


Figure 2—Integration count begins when the falling voltage ramp passes through zero and ends after 8192 counts. The deintegration count then begins, ending only when the rising voltage ramp again passes through zero.

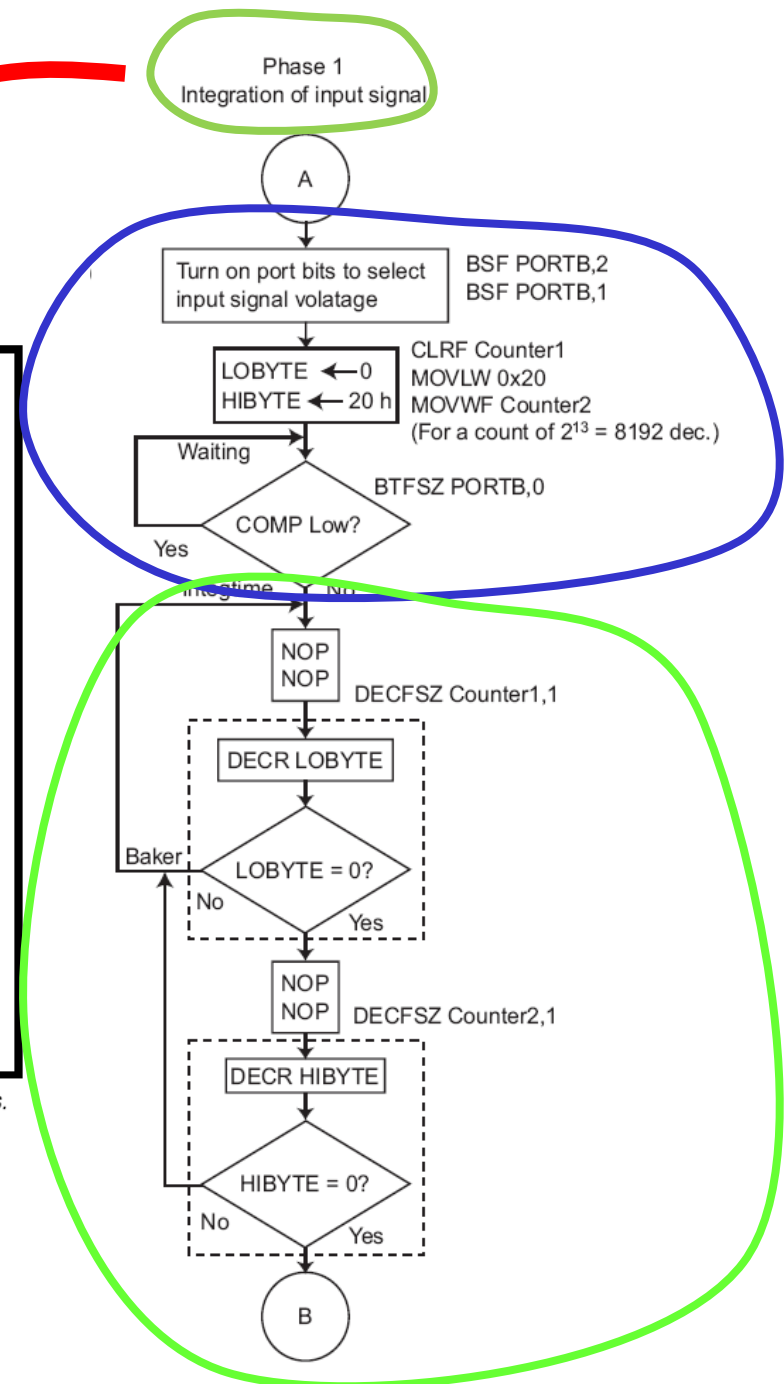

# ADC doble rampa



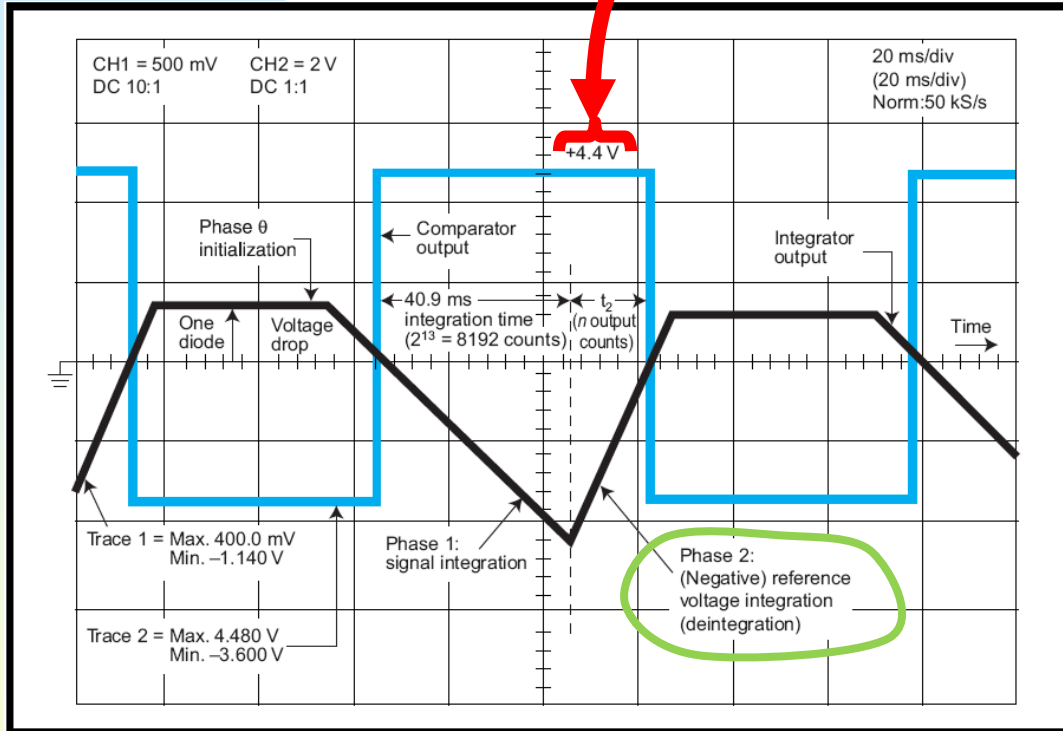


Figure 2—Integration count begins when the falling voltage ramp passes through zero and ends after 8192 counts. The deintegration count then begins, ending only when the rising voltage ramp again passes through zero.

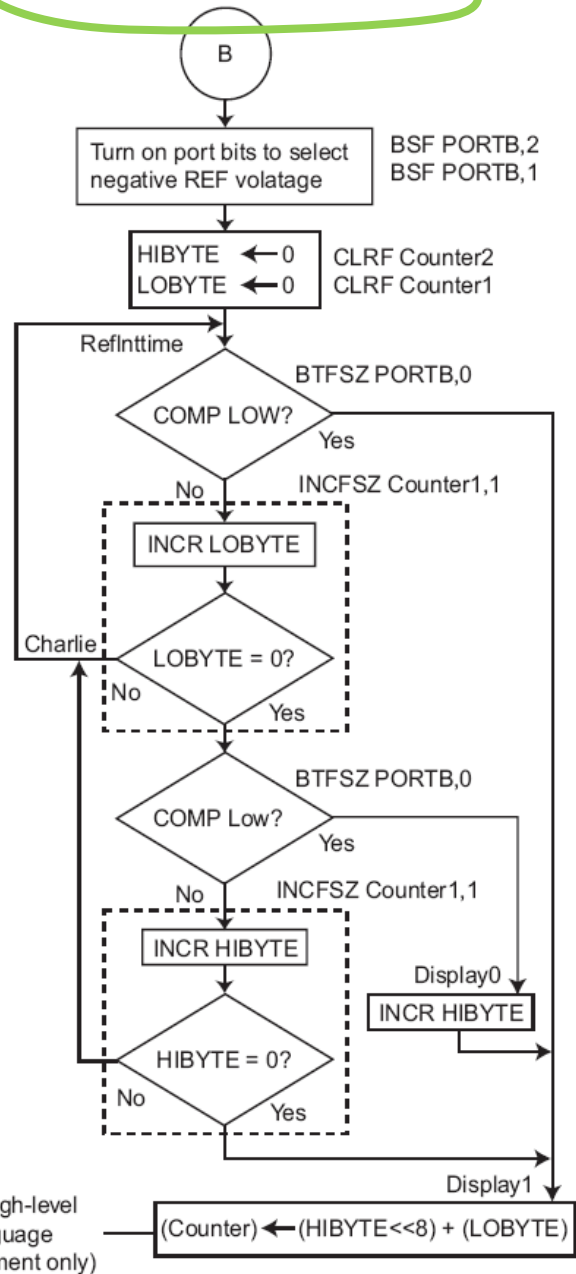Phase 2  
Integration of negative reference voltage




# ADC Flash

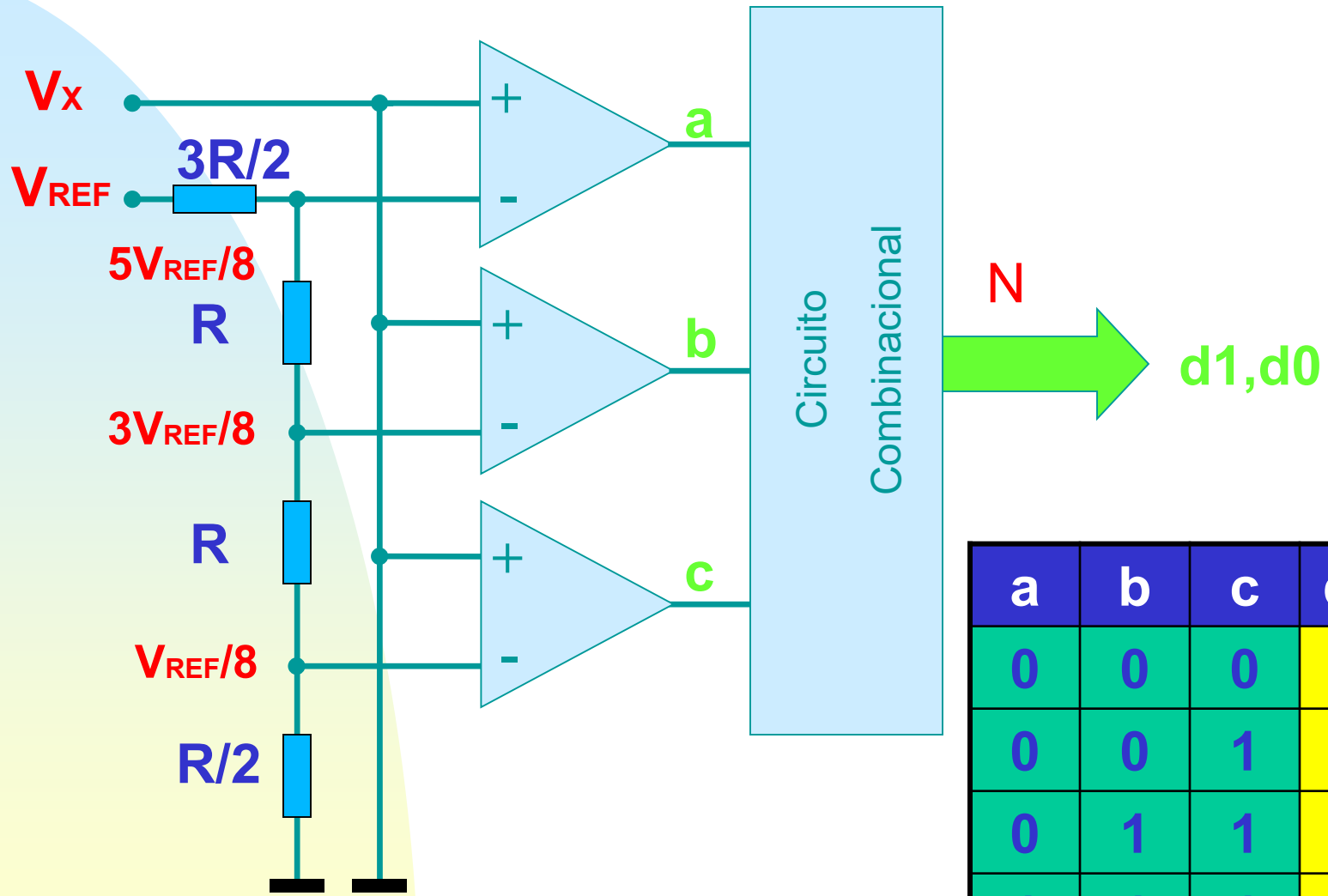

Simulación


a	b	c	d1	d0
0	0	0	0	0
0	0	1	0	1
0	1	1	1	0
1	1	1	1	1

# ADC Half-Flash

 

Simulación

# ADC Half-Flash

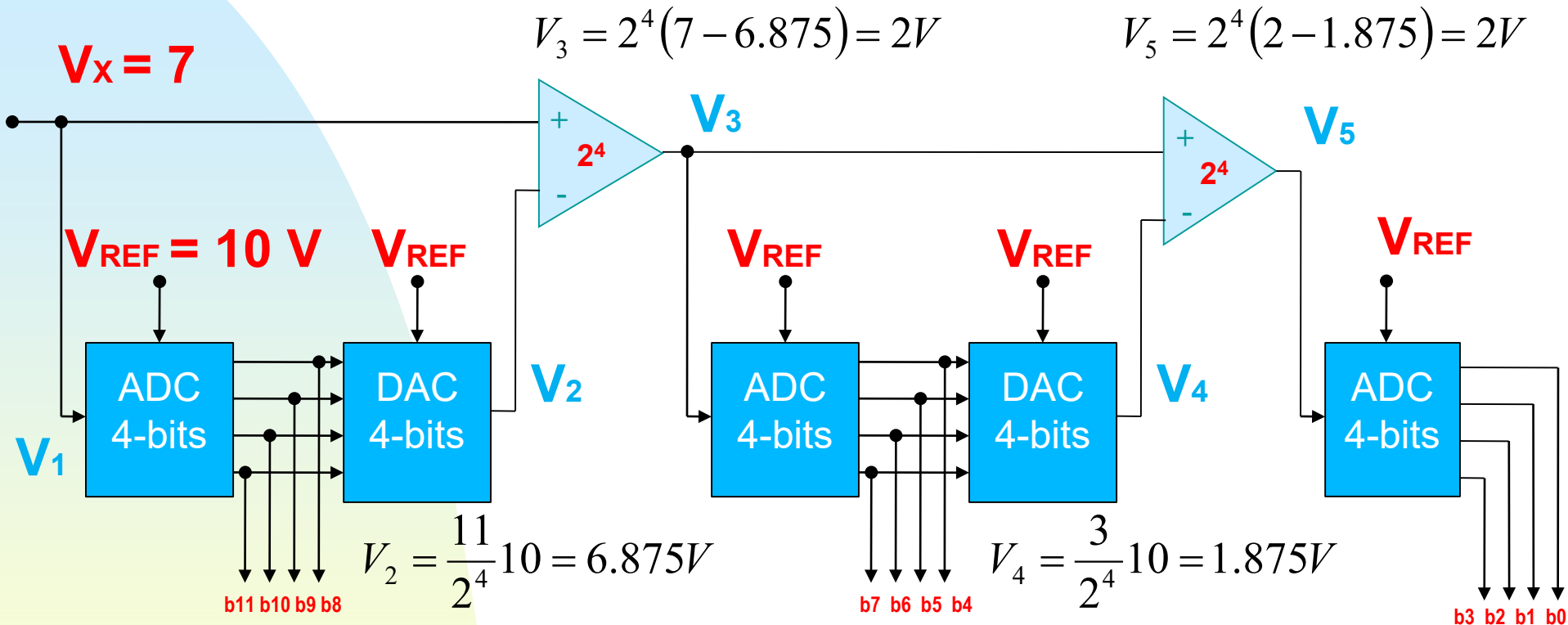

$$N = \text{trunc}\left(\frac{7}{10} 2^4\right) = 11$$

$$N = \text{trunc}\left(\frac{2}{10} 2^4\right) = 3$$

$$N = \text{trunc}\left(\frac{2}{10} 2^4\right) = 3$$

$$N = \text{trunc}\left(\frac{7}{10} 2^{12}\right) = 2867 = B33_{16}$$


# ADC Sigma-Delta

## Modulación Delta:

- La señal analógica es cuantificada por un ADC de 1 bit (Comparador)
- La salida del comparador es nuevamente convertida a una señal analógica con un DAC de 1 bit
- y restada de la entrada, tras pasar por un integrador
- La forma de la señal analógica es transmitida así:
  - Un “1” indica que ha habido una variación positiva desde la última muestra
  - Un “0” indica que ha habido una variación negativa desde la última muestra




# ADC Sigma-Delta

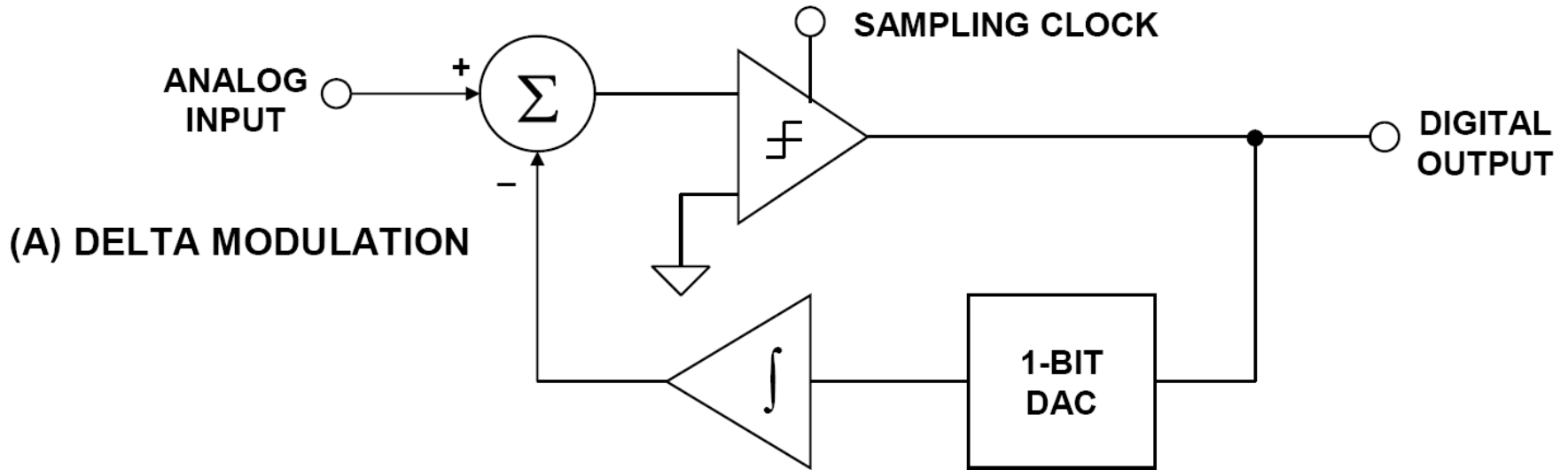

<http://designtools.analog.com/dt/sdtutorial/sdtutorial.html>

# ADC Sigma-Delta

 

**Figure 2: Quantization Using Delta Modulation**

# ADC Sigma-Delta

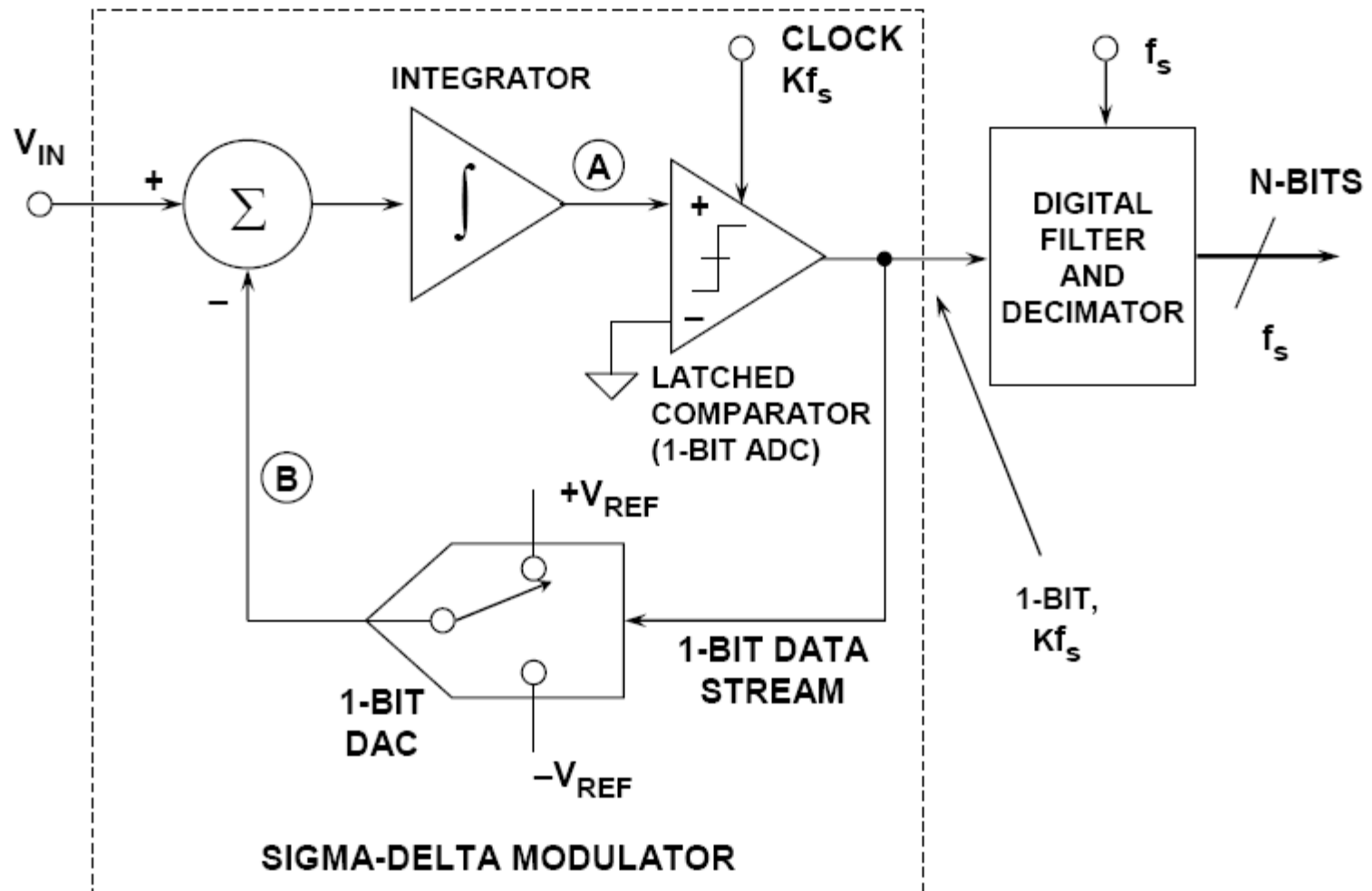



Figure 4: First-Order Sigma-Delta ADC

# ADC Sigma-Delta

$$V_{IN} = 0V$$

$$= \frac{2}{4}$$


$$= \frac{4}{8}$$

 

$$V_{IN} = + \frac{V_{ref}}{2}$$


$$= \frac{3}{4}$$

$$= \frac{6}{8}$$

 

*Figure 5: Sigma-Delta Modulator Waveforms*

# ADC Sigma-Delta

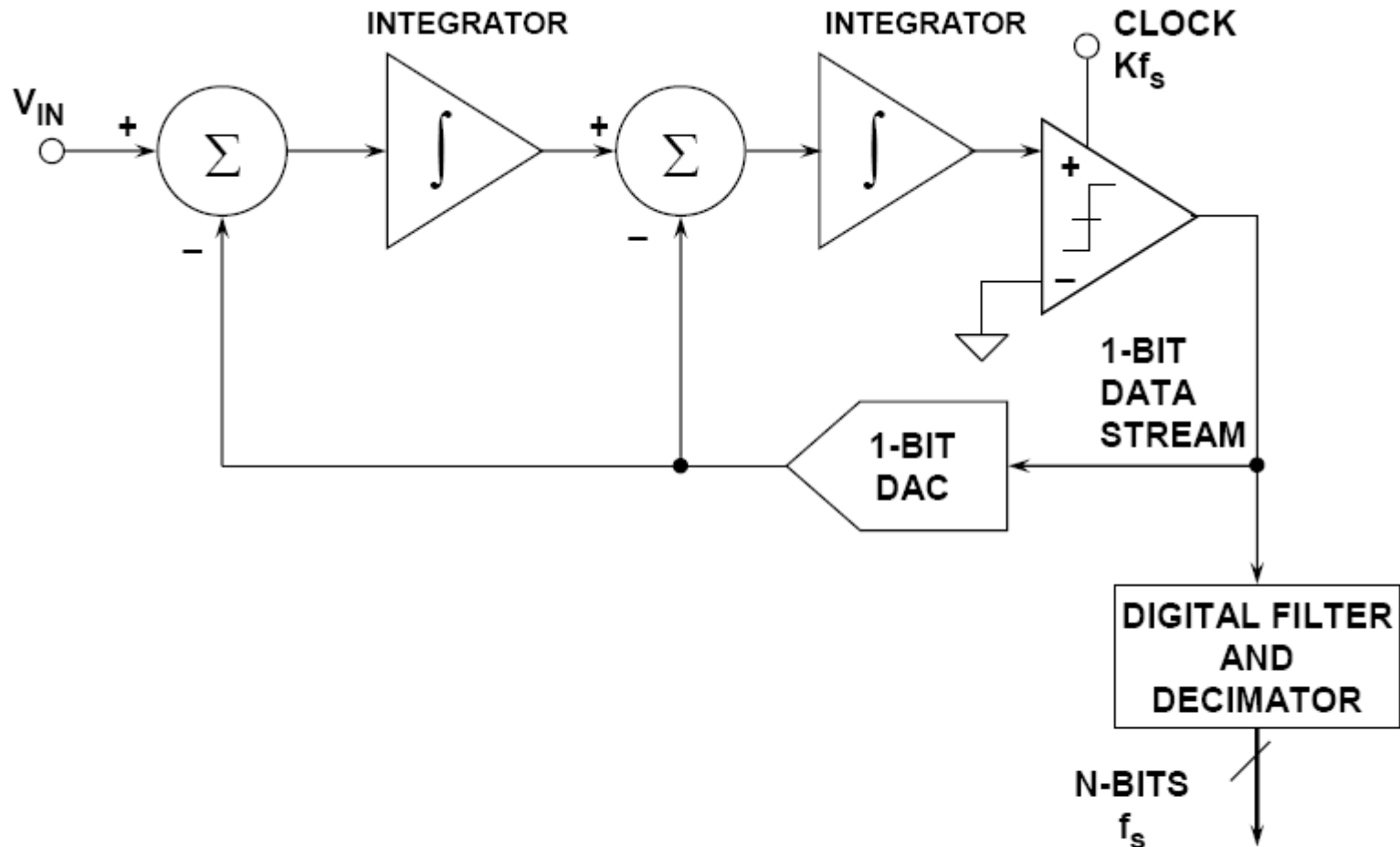

**Figure 8: Second-Order Sigma-Delta ADC**

# ADC Comparación


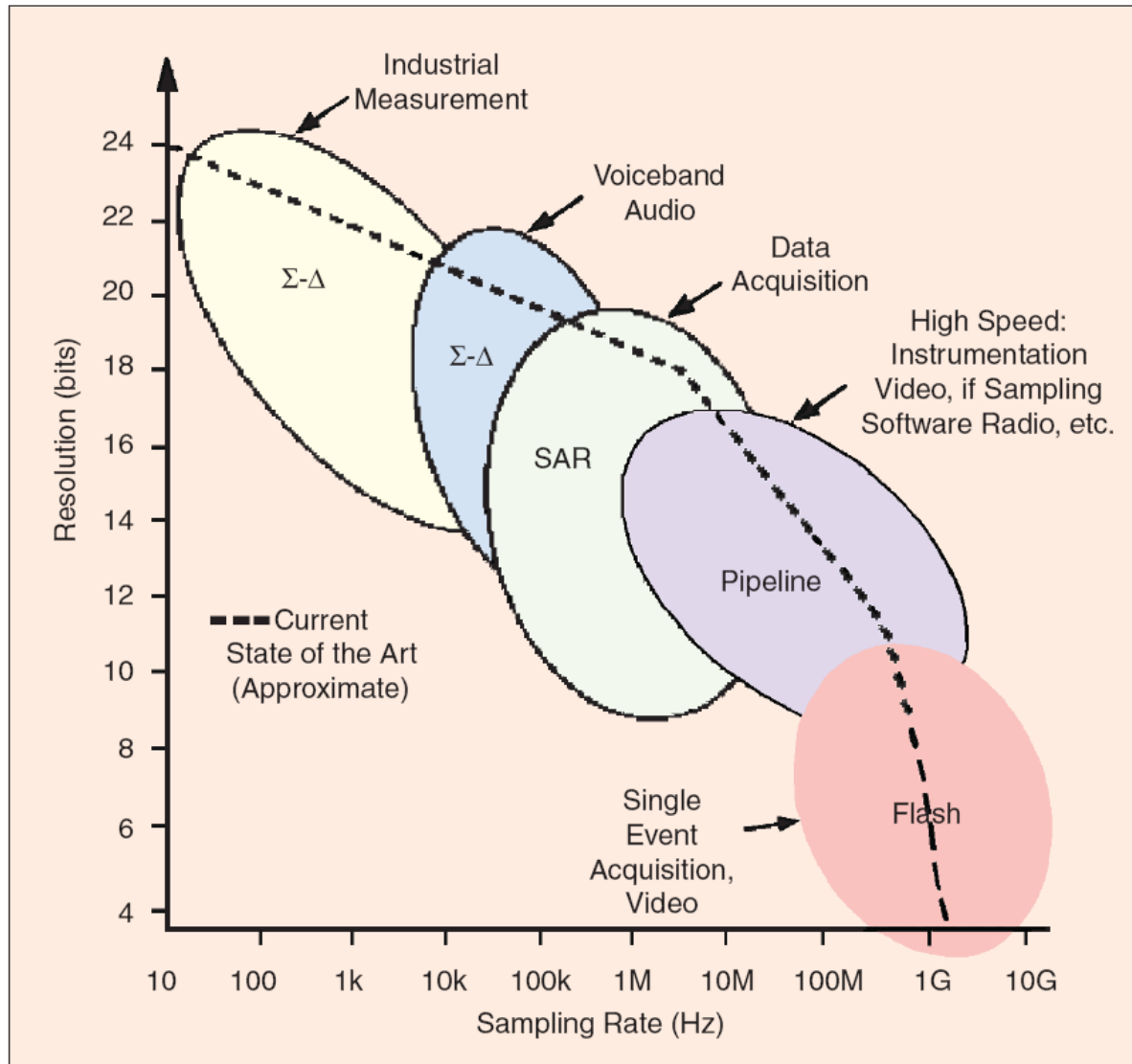



Fig. 1. ADC architectures, applications, resolution, and sampling rates.

# ADC: Error de cero

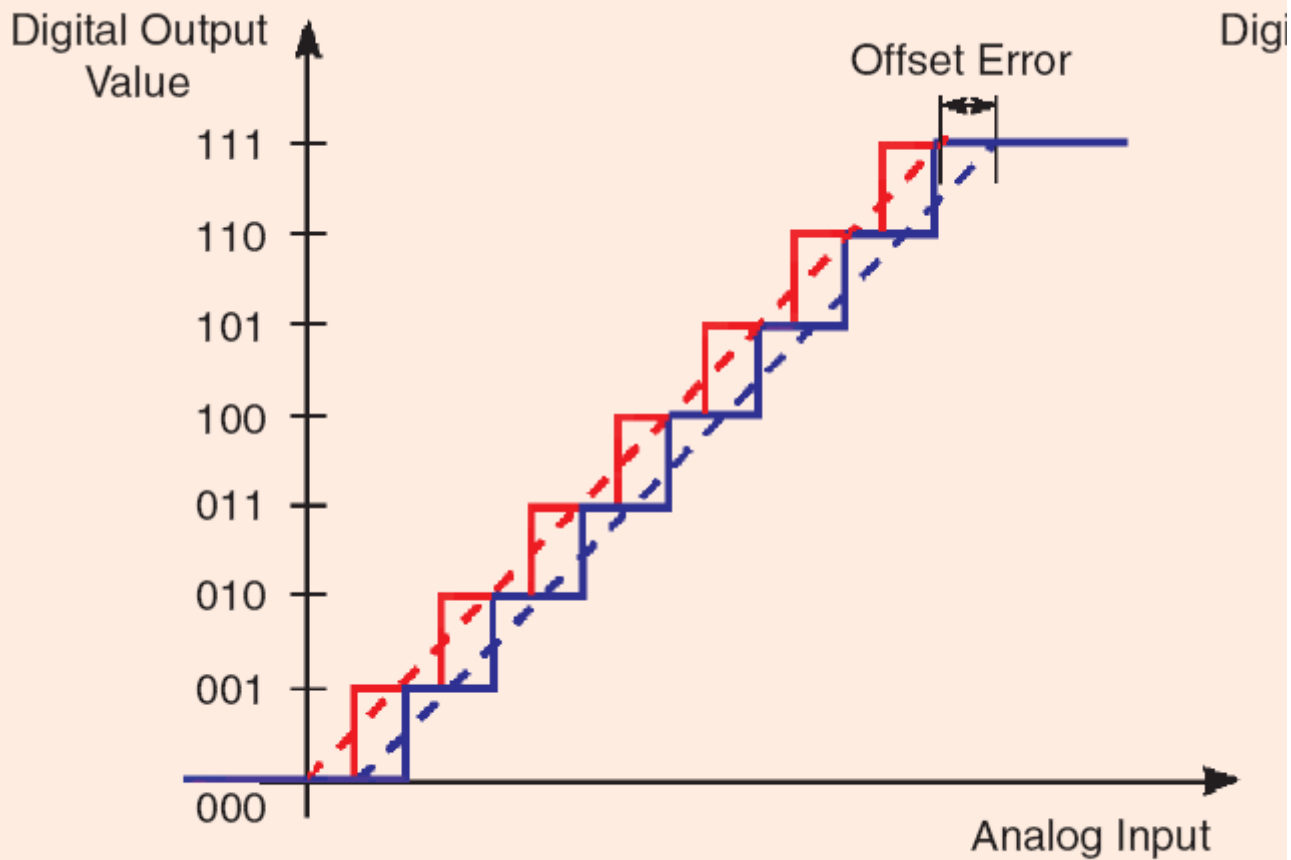

(a)

# ADC: Error de ganancia

 




# ADC: Errores de cero y de ganancia

## GAIN AND OFFSET ERRORS

Gain and offset errors represent the error contribution due to the displacement of the actual ADC characteristic from the reference one. The reference characteristic can be chosen according to several criteria. Most commonly used are the following:


- ▶ *Endpoint criterion*: the gain and offset errors are corrected such that the first and the last transition levels correspond exactly to the ideal ones.
- ▶ *Least square criterion*: the gain and offset errors are corrected such that the mean square deviation from the nominal reference transition levels are minimized.

# ADC: Error No Linealidad Integral

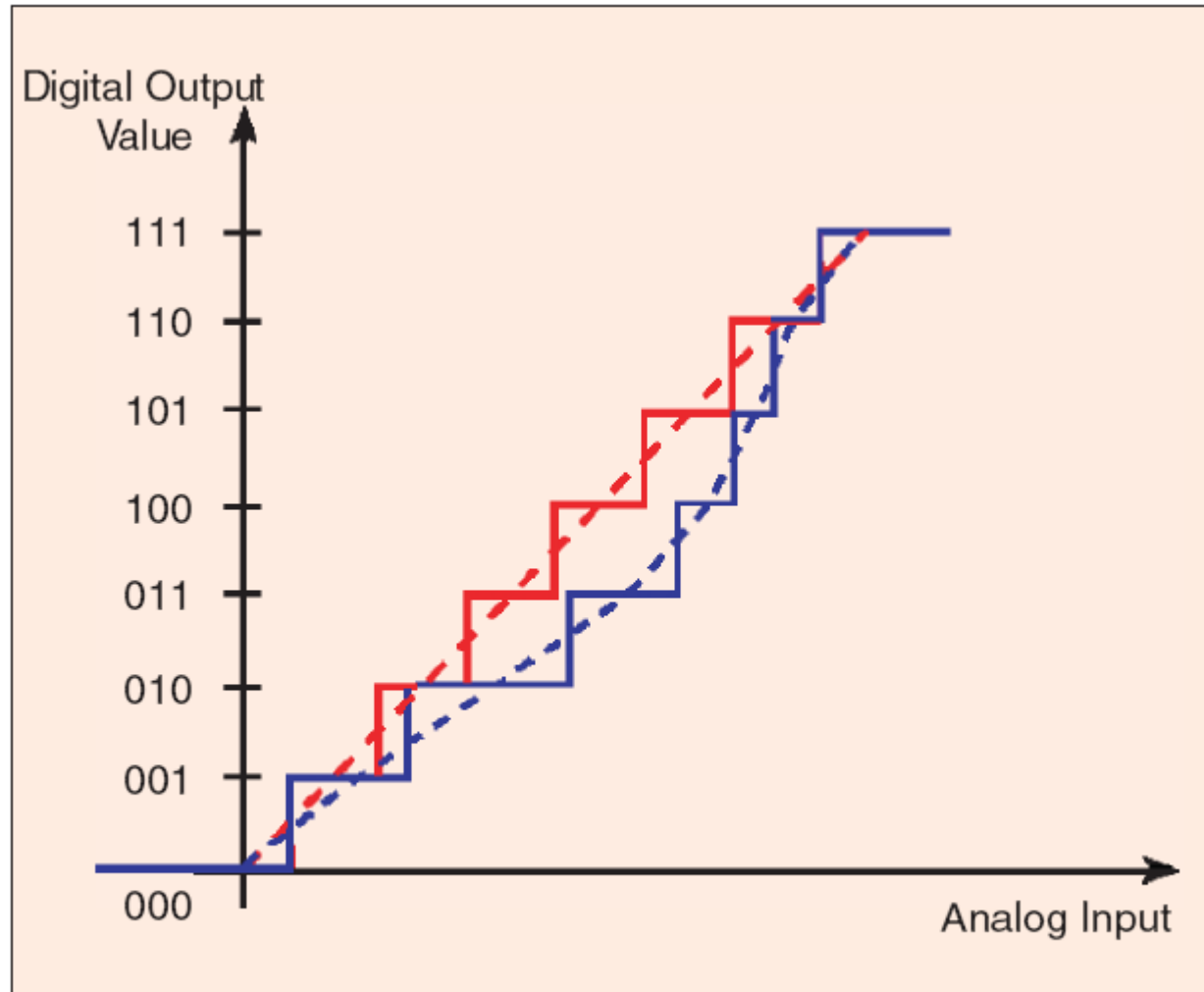

**Fig. 10.** INL causes the curve joining the middle point of each quantization step to not be a straight line.

# ADC: Monotonicidad

 


*Fig. 11.* The sample characteristic of a nonmonotonic ADC.

# ADC: Monotonicidad

## **MONOTONICITY**

An ADC is said to be monotonic if an increase or a decrease of the analog input signal correspond in every case to an increase or a decrease of the average digital output code (Figure 11). Such property is very relevant in applications where the stability is a key factor, such as in automatic control, where some variables are continuously tuned.

# ADC: Histéresis

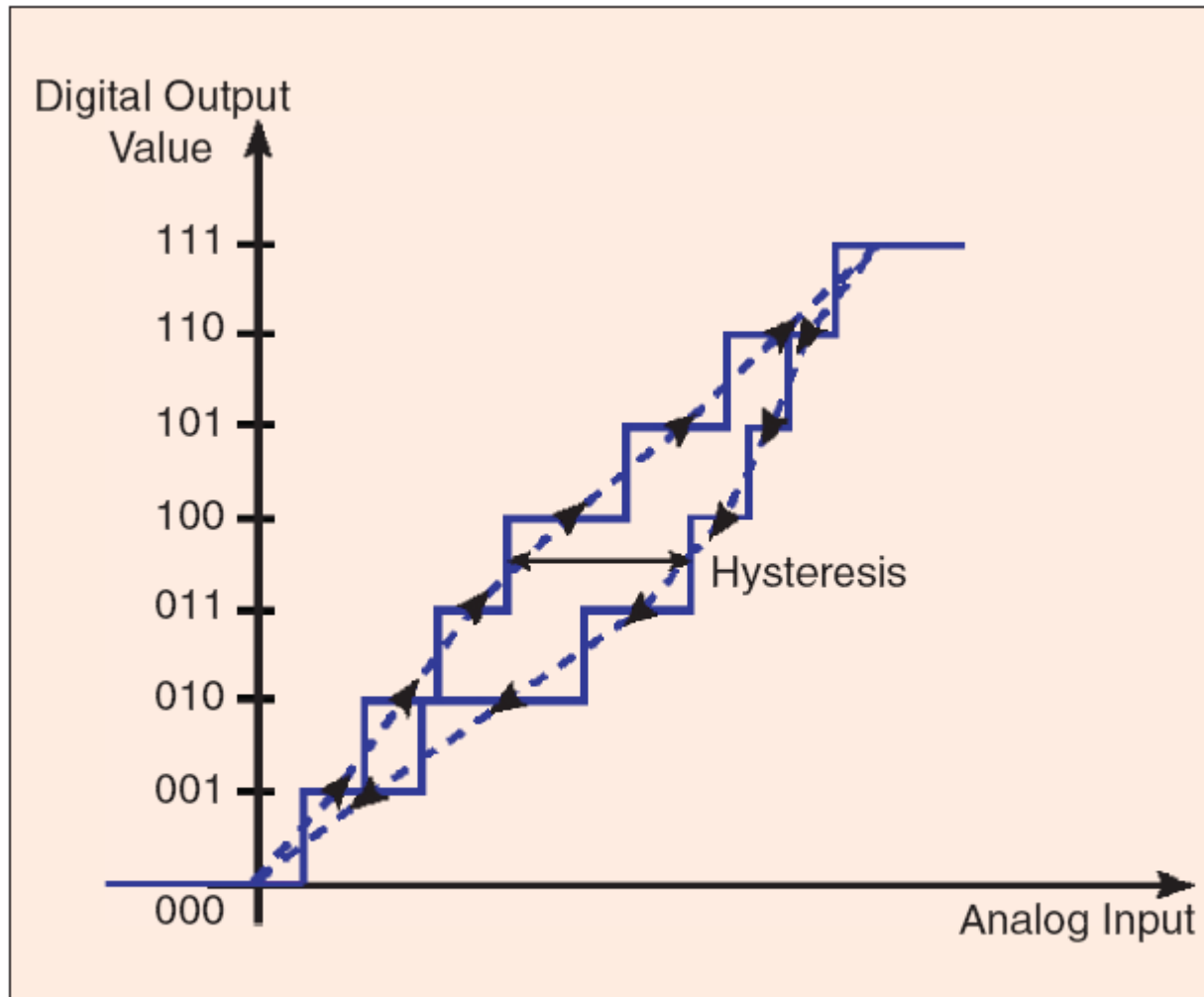

**Fig. 12.** The hysteresis shown on the characteristic.

# ADC: Histéresis

## **HYSTERESIS**

ADC characteristics often change when the slope of the input signal changes. In particular, two different curves can be observed when the input signal is increasing and decreasing. The hysteresis of an ADC is defined to be the maximum deviation of the transition levels (Figure 12). Hysteresis can be present at isolated code transitions. Hysteresis (and its complement, alternation) is evidence of feedback from previous ADC outputs into the input.

# ADC: Errores y Especificaciones

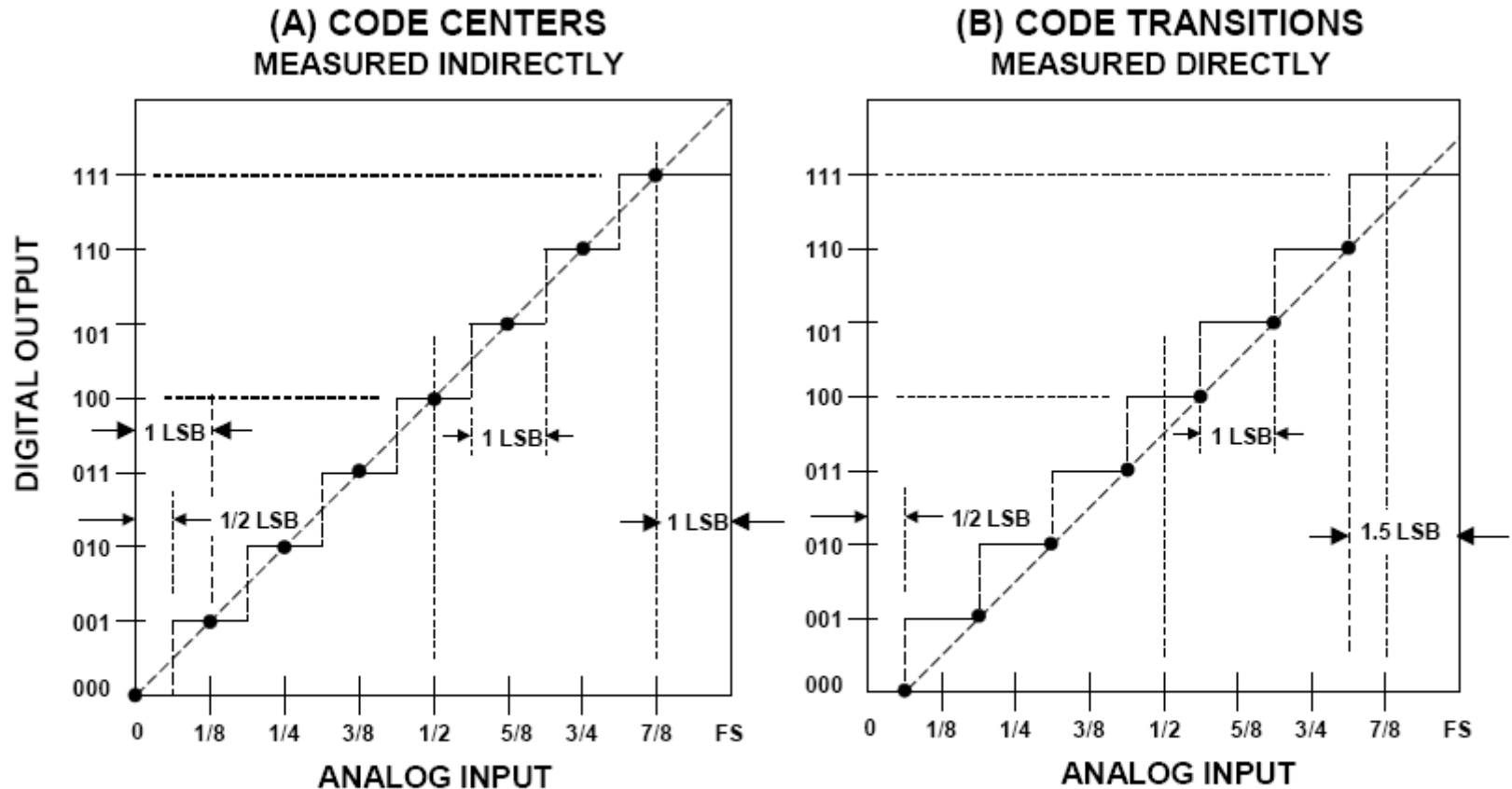


Figure 5.26: Measuring ADC Code Transitions to Determine Code Centers

# ADC: Errores Offset y Ganancia


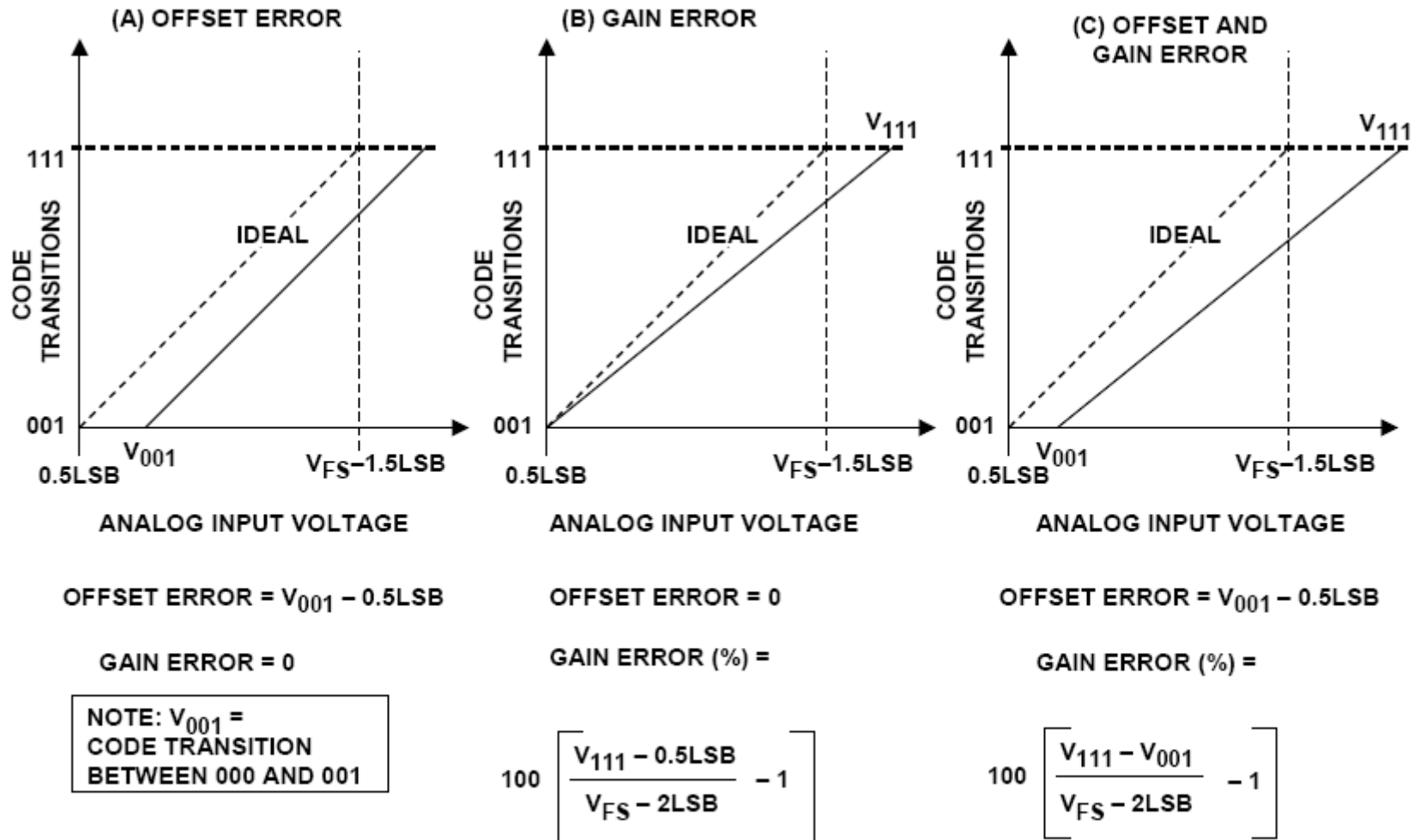


Figure 5.29: Measuring ADC Offset and Gain Error

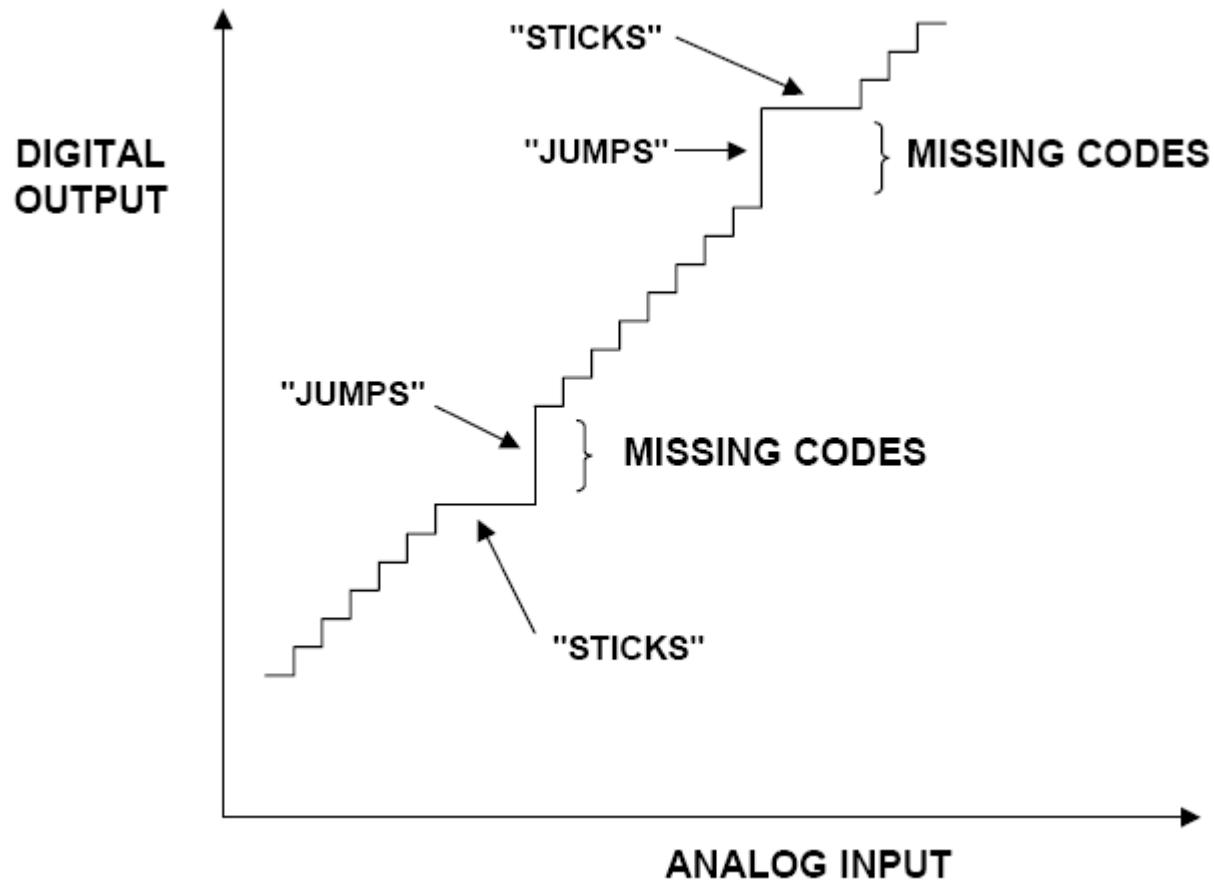

# ADC: Missing Codes



# ADC: Selección

- <http://www.analog.com/en/analog-to-digital-converters/ad-converters/products/index.html>
- <http://www.ti.com/lscs/ti/data-converters/analog-to-digital-converter-products.page>
- <http://www.microchip.com/pagehandler/en-us/products/analog/dataconverters/home.html>